



ISPIT IZ OSNOVA ELEKTRONIKE
modul: ELK, EKM, EEN, US i T

Zadaci

1. Zadatak: Izmereno je da napon na izlazu pojačavača opadne za 20% kada mu se priključi potrošač od $1k\Omega$. Kolika je izlazna otpornost pojačavača?

$$V_i = \frac{R_p}{R_i + R_p} V_{i0} = 0.8 \cdot V_{i0} \Rightarrow \frac{R_p}{R_i + R_p} = 0.8$$

$$R_p = 0.8 \cdot (R_i + R_p) \Rightarrow R_i = \frac{0.2}{0.8} R_p = 0.25 R_p = 250\Omega \quad 100\%$$

2. Zadatak: Za kolo sa Sl. 2 odrediti:


- jednosmernu struju drena svih tranzistora,
- parametre modela za male signale (g_m , r_o) svih tranzistora i
- otpornost, R_o .

Poznato je: $R_1=65k\Omega$, $R_2=35k\Omega$, $V_{DD}=3.3V$, $V_A \approx 1/\lambda$.

Parametri tranzistora su:

$A_k=100\mu A/V^2$, $V_{THk}=500mV$, $V_{Ak}=80V$, $k=1,2,3,4$,

$A_n=70\mu A/V^2$, $V_{THn}=450mV$, $V_{An}=60V$, $n=5,6$.

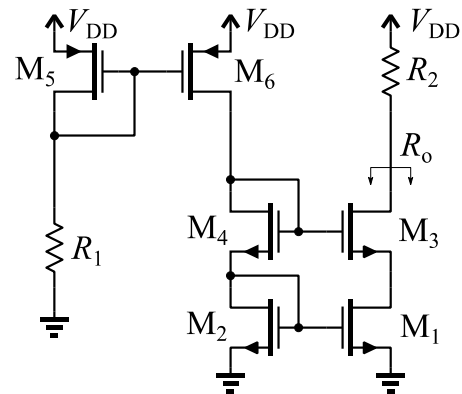

Sl. 2

a)

$$V_{DD} = V_{SG5} + I_{D5} R_1$$

$$V_{DD} - V_{TH5} = V_{SG5} - V_{TH5} + A_5 R_1 (V_{SG5} - V_{TH5})^2$$

$$A_5 R_1 V_{ov5}^2 + V_{ov5} - (V_{DD} - V_{TH5}) = 0 \quad 25\%$$

$$V_{ov5} = \frac{-1 + \sqrt{1 + 4A_5 R_1 (V_{DD} - V_{TH5})}}{2A_5 R_1} = 0.689V \quad 10\%$$

$$I_{D5} = A_5 V_{ov5}^2 = 33.23\mu A, I_{D1} = I_{D2} = I_{D3} = I_{D4} = I_{D6} = I_{D5} \quad 10\%$$

b)

$$g_{m5} = \frac{2I_{D5}}{V_{ov5}} = 96.46\mu S, g_{m5} = g_{m6}, g_{m1} = \frac{2I_{D1}}{V_{ov1}} = 115.292\mu S, g_{m1} = g_{m2} = g_{m3} = g_{m4} \quad 10\%$$

$$r_{o5} = \frac{V_{A5}}{I_{D5}} = 1.805M\Omega, r_{o5} = r_{o6}, r_{o1} = \frac{V_{A1}}{I_{D1}} = 2.407M\Omega, r_{o1} = r_{o2} = r_{o3} = r_{o4} \quad 10\%$$

c)

$$\begin{bmatrix} \left(\frac{1}{r_{o1}} + \frac{1}{r_{o3}} + g_{m3}\right) & -\frac{1}{r_{o3}} \\ -\frac{1}{r_{o3}} - g_{m3} & \frac{1}{r_{o3}} \end{bmatrix} \begin{bmatrix} v_{d1} \\ v_o \end{bmatrix} = \begin{bmatrix} 0 \\ i_o \end{bmatrix} \quad 25\%$$

$$R_o = \frac{v_o}{i_o} = r_{o3} + (1 + g_{m3} r_{o3}) r_{o1} = 673.013M\Omega \quad 10\%$$


3. Zadatak

Za kolo pojačavača sa Sl. 3 odrediti:

a) Jednosmerni napon na bazi tranzistora, V_B ;

b) Naponsko pojačanje $A_n = \frac{V_{iz}}{V_g}$.

Deo kola koji predstavlja izvor konstantne struje prikazan je kao idealni jednosmerni strujni generator I . Parametri tranzistora su: $h_{11E} = r_\pi = 2,5 \text{ k}\Omega$; $h_{21E} = \beta = 100$; $g_m = \beta/r_\pi = 40 \text{ mS}$; $V_{BE} = 0,7 \text{ V}$. Poznato je $R_B = 100 \text{ k}\Omega$; $R_C = 8 \text{ k}\Omega$; $R_g = R_p = 5 \text{ k}\Omega$; $I = 1 \text{ mA}$; $V_{CC} = V_{EE} = 12 \text{ V}$; $C_S \rightarrow \infty$.

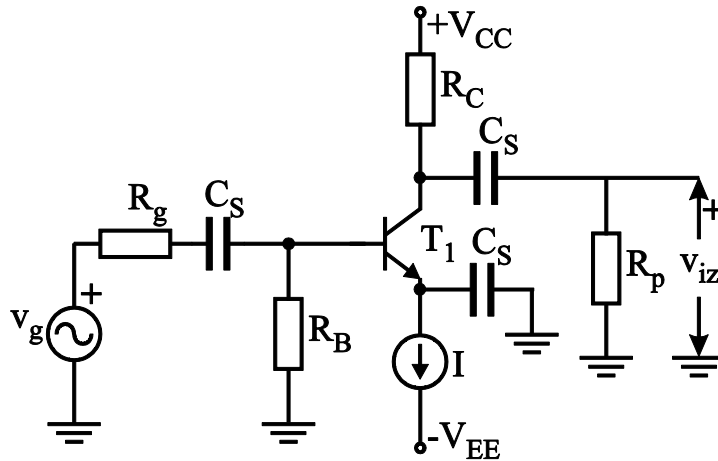


Sl. 3

a)

$$I_E = I = (1 + \beta)I_B$$

$$V_B = -R_B I_B = -R_B \frac{I}{1 + \beta} = -0,99 \text{ V}$$

b)

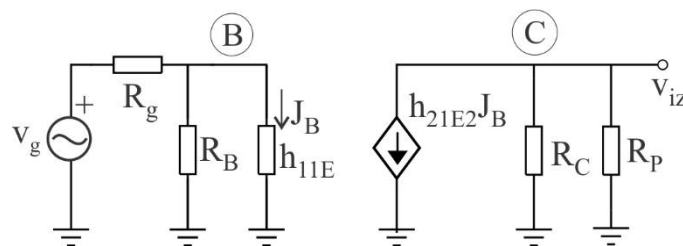

$$J_B = \frac{v_B}{h_{11E}}$$

$$\frac{1}{h_{11E}} \cdot v_B + \frac{1}{R_B} \cdot v_B + \frac{1}{R_g} \cdot (v_B - v_g) = 0$$

$$h_{21E} \cdot J_B + \frac{1}{R_C} \cdot v_{iz} + \frac{1}{R_P} \cdot v_{iz} = 0$$


$$A_n = \frac{v_{iz}}{v_g} = \frac{-h_{21E} \cdot R_C || R_P \cdot R_B}{R_B \cdot h_{11E} + R_g \cdot R_B + R_g \cdot h_{11E}} = -40,3$$

4. Zadatak

U kolu sa Sl. 4 upotrebljen je idealizovani pojačavač sa $A=100\text{dB}$. Odrediti:

- R_2/R_1 tako da se dobije $A_r=50$,
- β u dB,
- napon na izlazu V_o i V_- ukoliko je $V_s=0.1\text{V}$,
- za koliko će se smanjiti A_r ukoliko pojačanje A opadne za 20%?

Idealizovani pojačavač ima beskonačnu ulaznu i nultu izlaznu otpornost.

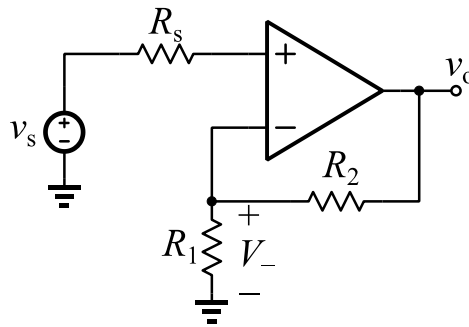

Sl. 4

- a) Odrediti R_2/R_1 tako da se dobije $A_r=100$!

$$A_r = \frac{A}{1-AB} = 50 \text{ za } AB \gg 1 \Rightarrow -\frac{1}{B} = 50$$

$$B = \frac{V_-}{V_o} = -\frac{R_1}{R_1 + R_2}$$

$$-\frac{1}{B} = \frac{R_1 + R_2}{R_1} = 1 + \frac{R_2}{R_1} = 50 \Rightarrow \frac{R_2}{R_1} = 49$$

- b) Odrediti B u dB?

$$B = 20 \log\left(\frac{1}{50}\right) = 20 \log(0.02) = -33,8\text{dB}$$

- c) Odrediti napon na izlazu V_o , i V_- ukoliko je $V_s=0.1\text{V}$.

$$V_o = \frac{A}{1-AB} V_s = 50 \cdot 0.1\text{V} = 5\text{V}$$

$$V_- = \frac{R_1}{R_1 + R_2} V_o = 5\text{V} / 50 = 0.1\text{V}$$

- d)

Odrediti za koliko će se smanjiti A_r ukoliko pojačanje A opadne za 20%?

$$A_r = \frac{A}{1-AB} = 50; \quad A_r' = \frac{0.8A}{1-0.8AB}$$

$$\frac{A_r - A_r'}{A_r} \cdot 100 = \left(1 - \frac{0.8A}{\frac{A}{1-AB}} \right) \cdot 100$$

$$\frac{A_r - A_r'}{A_r} \cdot 100 = 0,0122\%$$

Predmetni nastavnici