



OSNOVI ELEKTRONIKE

Zadaci

1. Za diodno kolo sa Sl. 1 odrediti i nacrtati zavisnost:


- a) izlaznog napona, V_i , i
b) ulazne struje, I_u , u funkciji ulaznog napona V_u .

Poznato je:

$R_1=1\text{k}\Omega$, $R_2=2\text{k}\Omega$, $V_2=3\text{V}$ i $-12\text{V} \leq V_u \leq 12\text{V}$.

Parametri modela diode su:

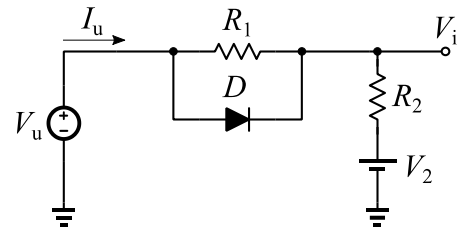$V_{D0}=0.6\text{V}$, $r_d=0\Omega$.

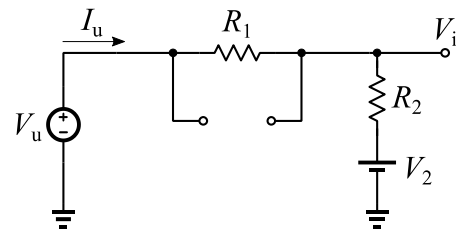


Sl. 1

Dioda ne vodi za $-12\text{V} \leq V_u < V_i + V_{D0} = 4.8\text{V}$, **10%**

$$V_i = \frac{R_2}{R_2 + R_1} V_u + \frac{R_1}{R_1 + R_2} V_2 = \frac{2}{3} V_u + 1 [\text{V}] \quad \mathbf{5\%}$$




$$I_u = \frac{1}{R_2} (V_i - V_2) = \frac{1}{3} V_u - 1 [\text{mA}] \quad \mathbf{5\%}$$

**10%**

Dioda vodi za $V_i + V_{D0} = 4.8\text{V} \leq V_u < 12\text{V}$, **10%**

$$V_i = V_u - V_{D0} = V_u - 0.6 [\text{V}] \quad \mathbf{5\%}$$

$$I_u = \frac{1}{R_2} (V_i - V_2) = \frac{1}{2} V_u - 1.8 [\text{mA}] \quad \mathbf{5\%}$$

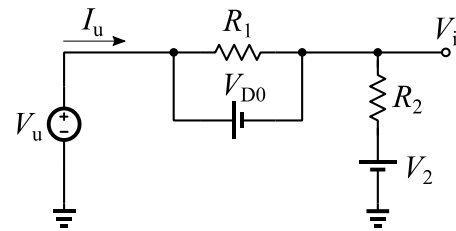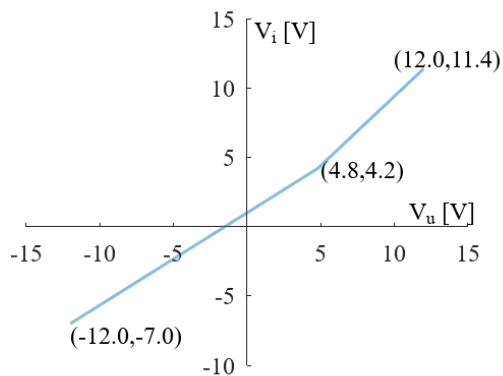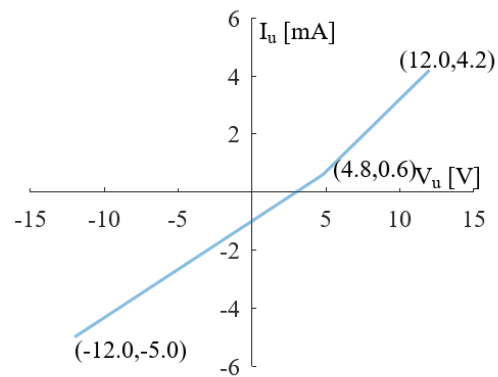**10%****20%****20%**

2. Za pojačavač sa Sl. 2 odrediti:

- parametre modela za male signale, g_m i r_π ,
- naponsko pojačanje, $A_n = v_p/v_u$ i
- ulaznu otpornost, R_{ul} .


Poznato je:

$R_1=50k\Omega$, $R_2=140k\Omega$, $R_3=1k\Omega$, $R_u=50\Omega$, $R_p=1k\Omega$,
 $V_{CC}=10V$.

Parametri tranzistora su:

$\beta = 100$, $V_{BE} = 0.6V$, $V_A \rightarrow \infty V$.

Smatrati da su kapacitivnosti sprežnih kondenzatora, C_S , izuzetno velike.

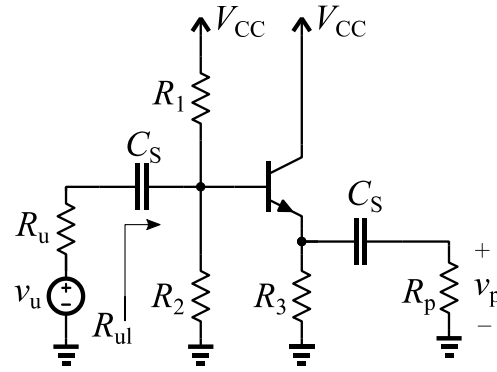


Sl. 2

a)

$$V_{BB} = V_{CC} \cdot \frac{R_2}{R_2 + R_1} = 7.368V, R_{BB} = R_1 || R_2 = 36.842k\Omega \quad \mathbf{10\%}$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_{BB} + (1 + \beta)R_3} = 49.103\mu A, I_C = \beta I_B = 4.910mA \quad \mathbf{10\%}$$
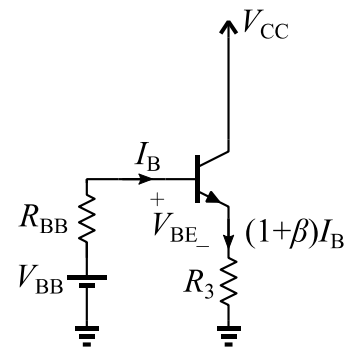
$$g_m = \frac{I_C}{V_T} = 196.411mS, r_\pi = 509.137\Omega \quad \mathbf{10\%}$$




10%

b)

$$v_{tev} = \frac{R_{BB}}{R_{BB} + R_u} v_u, R_{tev} = R_{BB} || R_u = 49.932\Omega \quad \mathbf{10\%}$$

$$R_L = R_3 || R_p = 500\Omega, R_b = r_\pi + (1 + \beta)R_L = 51.01k\Omega \quad \mathbf{10\%}$$
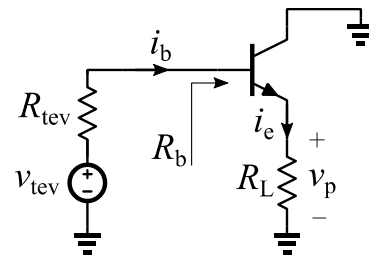
$$\begin{aligned} A_n &= \frac{v_p}{v_u} = \frac{v_p}{i_e} \cdot \frac{i_e}{i_b} \cdot \frac{i_b}{v_{tev}} \cdot \frac{v_{tev}}{v_u} \\ &= R_L \cdot (1 + \beta) \cdot \frac{1}{R_{tev} + R_b} \cdot \frac{R_{BB}}{R_{BB} + R_u} \\ &= 0.988 \quad \mathbf{10\%} \end{aligned}$$



10%

c)

$$R_{ul} = R_{BB} || R_b = 21.392 k\Omega \quad \mathbf{20\%}$$

3. Za kolo sa Sl. 3 odrediti:


- tip povratne sprege,
- faktor povratne sprege, F (β),
- prenosnu funkciju otvorene petlje, A ,
- naponsko pojačanje, A_{nr} , ulaznu, R_{ulr} , i izlaznu, R_{izr} , otpornost zatvorene petlje.

Poznato je:

$$R_1 = 10\text{k}\Omega, R_2 = 30\text{k}\Omega, R_L = 100\Omega.$$

Parametri modela operacionog pojačavača su:

$$A_o = 500\text{ V/V}, R_{uo} = 500\text{k}\Omega, R_{io} = 1\text{k}\Omega.$$

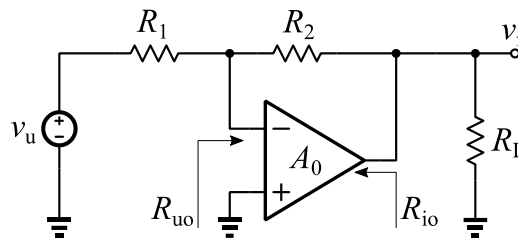

Sl. 3


- Paralelno-naponska **10%**

b)

$$F = \frac{i_v}{v_f} = -\frac{1}{R_2} = -33.333\mu\text{S} \quad \mathbf{10\%}$$

c)

$$i_u = \frac{v_u}{R_1}$$

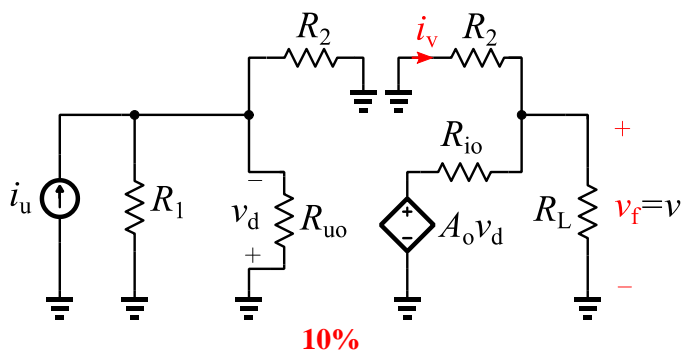

10%

$$A = \frac{v_i}{i_u} = \frac{v_i}{A_o v_d} \cdot \frac{A_o v_d}{v_d} \cdot \frac{v_d}{i_u} = \frac{R_L || R_2}{R_L || R_2 + R_{io}} \cdot A_o \cdot (-R_1 || R_2 || R_{uo}) = -334.856\text{k}\Omega \quad \mathbf{10\%}$$

d)

$$R_{ul} = R_1 || R_2 || R_{uo} = 7.389\text{k}\Omega, R_{ulr} = \frac{R_{ul}}{1 + AF} = 607.568\Omega \quad \mathbf{20\%}$$

$$R_{iz} = R_L || R_2 || R_{io} = 90.634\Omega, R_{izr} = \frac{R_{iz}}{1 + AF} = 7.452\Omega \quad \mathbf{20\%}$$

$$A_r = \frac{A}{1 + AF} = -27.533\text{k}\Omega, A_{nr} = \frac{v_i}{v_u} = \frac{v_i}{i_u} \cdot \frac{i_u}{v_u} = A_r \cdot \frac{1}{R_1} = -2.753 \frac{\text{V}}{\text{V}} \quad \mathbf{20\%}$$


4. Za oscilator sa Sl. 4 odrediti:

- determinantu sistema,
- frekvenciju oscilovanja, f_0 , i
- vrednost otpornosti, R_4 .

Poznato je:

$$R_1 = R_2 = R_3 = R = 10\text{k}\Omega, C_1 = C_2 = C_3 = C = 1\text{nF}.$$

Operacioni pojačavač je idealan.

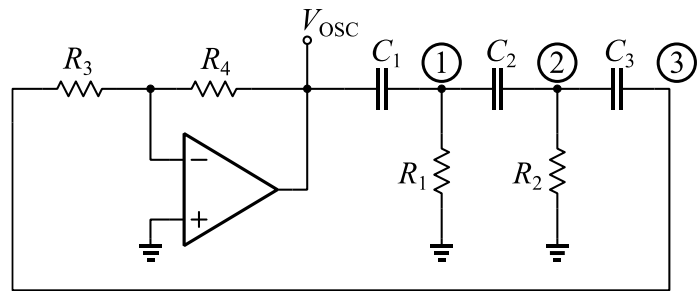

Sl. 4

$$V_{osc} = KV_3, K = -\frac{R_4}{R_3} \quad \mathbf{10\%}$$

$$\begin{bmatrix} s(C_1 + C_2) + \frac{1}{R_1} & -sC_2 & -KsC_1 \\ -sC_2 & s(C_2 + C_3) + \frac{1}{R_2} & -sC_3 \\ 0 & -sC_3 & sC_3 + \frac{1}{R_3} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} \quad \mathbf{30\%}$$

a)

$$\Delta = (s\tau)^3(1 - K) + 6(s\tau)^2 + 5s\tau + 1 = 0, \tau = RC = 10\mu\text{s} \quad \mathbf{20\%}$$

b)

$$\text{Re}\{\Delta\} = 1 - 6(\omega_o\tau)^2 = 0 \Rightarrow \omega_o = \frac{1}{\tau\sqrt{6}} = 4.082 \times 10^4 \frac{\text{rad}}{\text{sec}}, f_o = \frac{\omega_o}{2\pi} = 6.497\text{kHz} \quad \mathbf{20\%}$$

c)

$$\text{Im}\{\Delta\} = 5\omega_o\tau - (\omega_o\tau)^3(1 - K) = 0 \Rightarrow K = -29, R_4 = 29R = 290\text{k}\Omega \quad \mathbf{20\%}$$