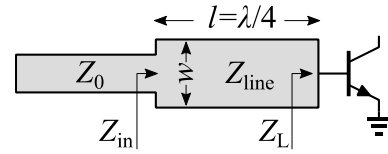




RF Elektronika

1. Tranzistor koji radi na frekvenciji, $f=3\text{GHz}$, ima ulaznu impedansu, $Z_L=50\Omega$. Za prilagođenje sa vodnom karakteristične impedanse, $Z_0=75\Omega$, upotrebljena je $\lambda/4$ transformator (Slika 1). Odrediti:



Slika 1

- karakterističnu impedansu, Z_{line} ,
- širinu, w , i
- dužinu, l , $\lambda/4$ transformatora.

Debljina dielektrika je $d=2\text{mm}$, a njegova realtivna dielektrična konstanta i magnetna permabilnost su $\epsilon_r=4.2$ i $\mu_r=1$. Poznato je, $c=3\cdot 10^8\text{ m/s}$, $\epsilon_0=8.84\cdot 10^{-12}\text{ F/m}$, $\mu_0=4\pi\cdot 10^{-7}\text{ H/m}$.

a) **40%**

$$\beta = \frac{2\pi}{\lambda}, l = \frac{\lambda}{4} \Rightarrow \beta l = \frac{\pi}{2}$$
$$Z_{in} = Z_0 = Z_{line} \frac{Z_L + jZ_{line} \tan(\beta l)}{Z_{line} + jZ_L \tan(\beta l)} = \frac{Z_{line}^2}{Z_L} \Rightarrow Z_{lin} = \sqrt{Z_0 Z_L} = 61.24\Omega$$

b) **40%**

$$Z_f = \sqrt{\frac{\mu_0}{\epsilon_0}} = 376.82\Omega$$
$$Z_{line} \approx \sqrt{\frac{L'}{C'}} = \sqrt{\frac{\mu_r \mu_0 \frac{d}{w}}{\epsilon_r \epsilon_0 \frac{w}{d}}} = Z_f \sqrt{\frac{\mu_r}{\epsilon_r}} \cdot \frac{d}{w} \Rightarrow w = d \cdot \frac{Z_f}{Z_{lin}} \cdot \sqrt{\frac{\mu_r}{\epsilon_r}} = 6.005\text{mm}$$


c) **20%**

$$v_p = \frac{c}{\sqrt{\epsilon_r \mu_r}}, \lambda = \frac{v_p}{f} = 48.795\text{mm} \Rightarrow l = \frac{\lambda}{4} = \frac{1}{4} \cdot \frac{v_p}{f} = 12.20\text{mm}$$

2. Na slici 2 prikazan je pojačavač klase C sa MOS-FET tranzistorom. Zavisnost struje drejana od napona gejtsors je data izrazom, $I_d = I_{dss}(U_{gs} - V_T)^2$, gde je $I_{dss} = 0.5A/V^2$ i $V_T = 1V$.
Odrediti:

- amplitudu prvog harmonika struje drejana,
- korisnu snagu P_{Rp} na potrošaču R_p i
- frekvenciju izlaznog signala, f_v , ako je širina propusnog ospega $B = 5MHz$.

Poznato je: $V_{g0} = 0.5V$, $U_{gm} = 1.5V$, $R_p = 50\Omega$, $\eta_{OK} = 80\%$, $L = 200nH$ i $\alpha_1(50^\circ) = 0.3388$, $\alpha_1(60^\circ) = 0.391$, $\alpha_1(70^\circ) = 0.4356$

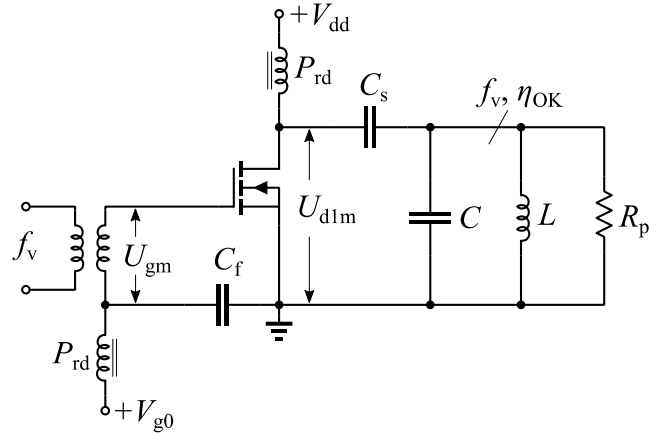

Slika 2

a) **40%**

$$e_g = u_g + V_{g0} \Rightarrow U_{gmax} = e_{gmax} = U_{gm} + V_{g0} = 4V$$

$$J_{dm} = I_{dm} = I_{dss}(U_{gmax} - V_T)^2 = 500.00mA$$

$$e_g(\theta_d) = U_{gm} \cos(\theta_d) + V_{g0} = V_T \Rightarrow \theta_d = \arccos\left(\frac{V_T - V_{g0}}{U_{gm}}\right) = 70.529^\circ \approx 70^\circ$$

$$J_{d1m} = \alpha_1(\theta_d)J_{dm} = 217.8mA$$

b) **40%**

$$R_d = R_{d0} || R_p$$

$$\eta_{OK} = \frac{P_{Rp}}{P_{uk}} = \frac{\frac{1}{2} \frac{U_{d1m}^2}{R_p}}{\frac{1}{2} \frac{U_{d1m}^2}{R_d}} = \frac{R_{d0}}{R_{d0} + R_p} \Rightarrow R_{d0} = R_p \frac{\eta_{OK}}{1 - \eta_{OK}} = 200\Omega$$

$$R_d = R_{d0} || R_p = 40\Omega, U_{d1m} = J_{d1m} R_d = 8.712V \Rightarrow P_{Rp} = \frac{1}{2} \frac{U_{d1m}^2}{R_p} = 758.989mW$$

b) **20%**


$$Q = \frac{R_d}{2\pi f_v L}, B = \frac{f_v}{Q} \Rightarrow f_v = \sqrt{\frac{R_d B}{2\pi L}} = 12.616MHz$$

3. Za AM detektor sa slike 3. Odrediti:

- ulaznu otpornost, R_{ul} ,
- detektovani jednosmerni napon, E_0 i
- amplitudu detektovanog NF napon, U_n , ako je stepen amplitudске modулacije $m = 45\%$.

Poznato je:

$$U_{AM} = 2V, \eta_d = 0.85, R_1 = 1k\Omega \text{ i } R_2 = 3k\Omega.$$

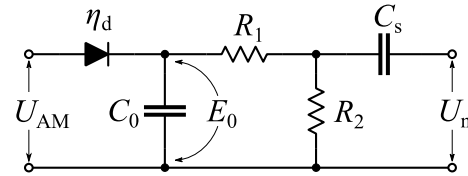

Slika 3

$$a) R_{ul} \approx \frac{R_1 + R_2}{2} = 2k\Omega \text{ 20\%}$$

$$b) \eta_d = \frac{E_0}{U_{AM}} \Rightarrow E_0 = \eta_d U_{AM} = 1.7V \text{ 20\%}$$

c)

$$U_{C_0, max} = U_{AM}(1 + m) = 1.1V, U_{C_0, min} = U_{AM}(1 - m) = 2.9V \text{ 20\%}$$

$$U_{C_0, pp} = U_{C_0, max} - U_{C_0, min} = 1.8V \text{ 20\%}$$

$$U_{C_0} = \frac{U_{C_0, pp}}{2} = 0.9V, U'_n = \eta_d U_{C_0} = 0.765V, U_n = \frac{R_2}{R_1 + R_2} U'_n = 573.75mV \text{ 20\%}$$

4. PLL sintetizator sa slike 4

sastoji se od:

- kvarcnog oscilatora, $f_Q = 1MHz$,
- pred-delitelja, $R = 800$,
- preskalera, $P = 400$, i
- programirljivog delitelja
($N_{min} - N_{max}$) = (1400 - 2600).

Odrediti:

a) korak (rezoluciju) u sintezi frekvencije, Δf , i

b) opseg frekvencija ($f_{0min} - f_{0max}$) u kome PLL sintetiše frekvencije.


a)

$$\Delta f_0 = f_q \frac{P}{R} = 500kHz \text{ 50\%}$$

b)

$$f_{0, min} = N_{min} \Delta f_0 = 700MHz \text{ 25\%}$$

$$f_{0, max} = N_{max} \Delta f_0 = 1300MHz \text{ 25\%}$$

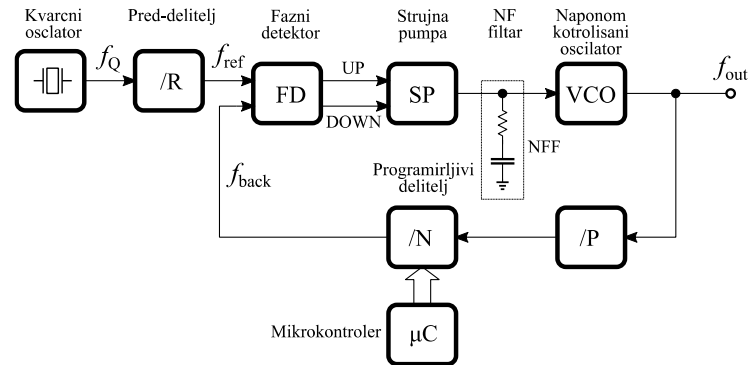

Slika 4