



## OSNOVI ELEKTRONIKE

Zadaci

1. Za diodno kolo sa Sl. 1 odrediti i nacrtati zavisnost:

a) izlaznog napona,  $V_i$ , i


b) ulazne struje,  $I_u$ , u funkciji ulaznog napona  $V_u$ .

Poznato je:

$R_1=R_2=2k\Omega$ ,  $V_2=4V$  i  $-10V \leq V_u \leq 10V$ .


Parametri modela diode su:

$V_{D0}=0.6V$ ,  $r_d=0\Omega$ .

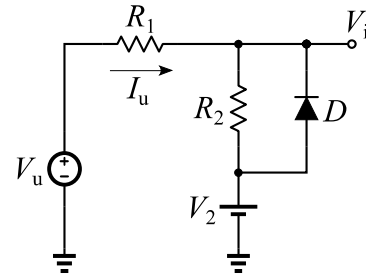

Sl. 1

Dioda vodi za,  $-10V \leq V_u < 2.8V$  **10%**

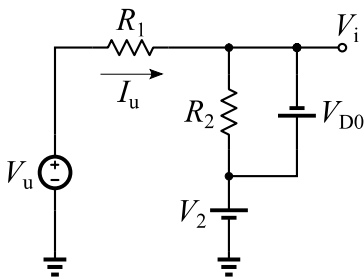
**10%**

$$V_i = -V_{D0} + V_2 = 3.4V$$

$$I_u = \frac{V_u - V_i}{R_1} = \frac{1}{2}V_u - 1.7mA$$



**10%**

Dioda ne vodi za,  $2.8V \leq V_u \leq 10V$  **10%**

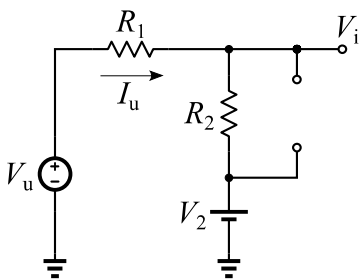**10%**

$$V_i = \frac{R_2}{R_2 + R_1} V_u + \frac{R_1}{R_2 + R_1} V_2 = \frac{1}{2} V_u + 2V$$

$$I_u = \frac{V_u - V_2}{R_1 + R_2} = \frac{1}{4} V_u - 1mA$$

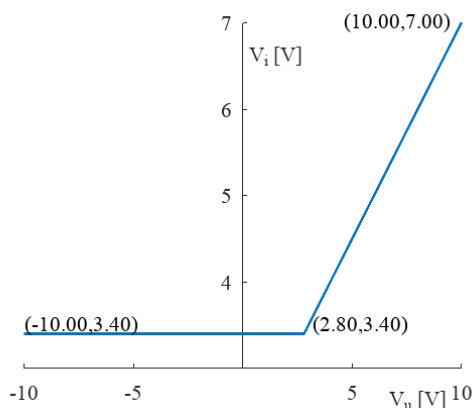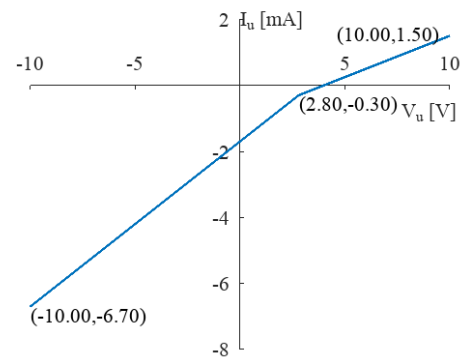**10%****20%****20%**

2. Za pojačavač sa Sl. 2 odrediti:

- a) parametre modela za male signale,  $g_m$  i  $r_0$ ,
- b) naponsko pojačanje,  $A_n = v_p/v_u$  i
- c) izlaznu otpornost,  $R_{iz}$ .


Poznato je:

$R_1=100k\Omega$ ,  $R_2=400k\Omega$ ,  $R_3=1.5k\Omega$ ,  $R_u=100\Omega$ ,  
 $R_p=5k\Omega$ ,  $V_{DD}=5V$ .


Parametri tranzistora su:

$A = 8mA/V^2$ ,  $V_{TH}=0.5V$ ,  $V_A=100V$ .

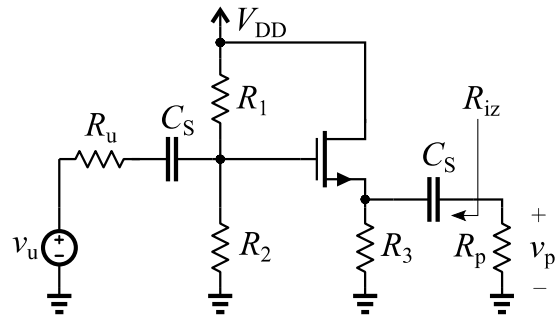Smatrati da su kapacitivnosti sprežnih kondenzatora,  $C_S$ , izuzetno velike.



a)

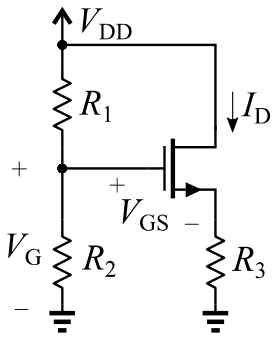

10%

$$V_G = V_{GS} + I_D R_3$$

$$V_G - V_{TH} = V_{GS} - V_{TH} + A (V_{GS} - V_{TH})^2 R_3$$

$$V_{ov} = V_{GS} - V_{TH}$$

$$A R_3 V_{ov}^2 + V_{ov} - (V_G - V_{TH}) = 0$$

$$V_{ov} = 0.5V \Rightarrow I_D = A V_{ov}^2 = 2mA \quad 10\%$$

$$g_m = 2A V_{ov} = 8mS, \quad r_0 = \frac{V_A}{I_D} = 50k\Omega \quad 10\%$$


b)

$$R_g = R_1 || R_2 = 80k\Omega$$

$$R_{tev} = R_g || R_u = 99.875\Omega$$

$$v_{tev} = \frac{R_g}{R_g + R_u} v_u = 0.9988 v_u$$

$$R_L = R_3 || R_p = 1.154k\Omega$$

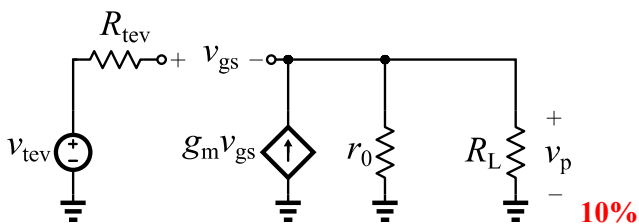


10%

$$EQ1 : v_{gs} = v_{tev} - v_p$$

$$EQ2 : v_p \frac{1}{R_L || r_0} - g_m v_{gs} = 0 \quad 20\%$$

$$A_n = \frac{v_p}{v_{tev}} \times \frac{v_{tev}}{v_u} = \frac{g_m (R_L || r_0)}{1 + g_m (R_L || r_0)} \times \frac{R_g}{R_g + R_u} = 0.899V/V \quad 10\%$$

c)

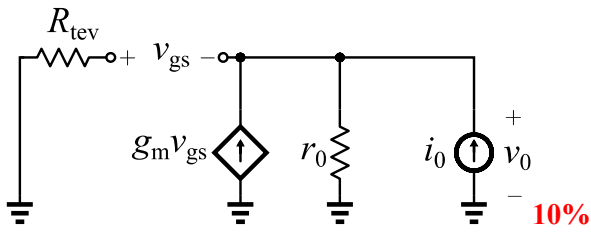

$$EQ1 : v_{gs} = -v_0$$

$$EQ1 : -i_0 - g_m v_{gs} + v_0 \frac{1}{r_0} = 0$$

$$R_T = \frac{v_0}{i_0} = \frac{r_0}{1 + \mu} = 124.69\Omega$$


$$R_{iz} = R_T || R_3 = 115.119\Omega \quad 20\%$$

3. Za kolo sa Sl. 3 odrediti:

- $v_x = f(v_1, v_2)$ ,
- diferencijalno pojačanje,  $A_d = v_i / (v_2 - v_1)$  i
- otpornost  $R_5$  tako da je  $A_d = 18$  V/V.

Poznato je:  $R_1 = R_2 = R_3 = R_4 = R = 15k\Omega$

Operacioni pojačavači su idealni.

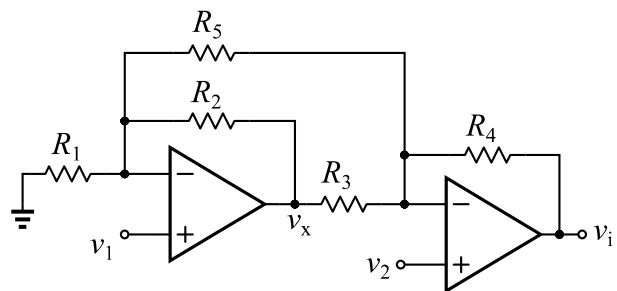

Sl. 3

a)

$$v_x = \left(1 + \frac{R_2}{R_5 || R_1}\right) v_1 - \frac{R_2}{R_5} v_2 \quad 30\%$$

b)

$$v_i = \left(1 + \frac{R_4}{R_5 || R_3}\right) v_2 - \frac{R_4}{R_3} v_x - \frac{R_4}{R_5} v_1$$

$$= \left(1 + \frac{R_4}{R_5 || R_3} + \frac{R_4 R_2}{R_3 R_5}\right) v_2 - \left(\frac{R_4}{R_5} + \frac{R_4}{R_3} \left(1 + \frac{R_2}{R_5 || R_1}\right)\right) v_1$$

$$A_d = \frac{v_i}{v_2 - v_1} = 3 + \frac{R}{R_5} \quad 50\%$$

c)

$$R_5 = \frac{R}{A_d - 3} = 15k\Omega \quad 20\%$$

4. Za regulator sa Sl. 4 odrediti:

- parametre modela za male signale,  $g_m$  i  $r_\pi$ ,
- osetljivost,  $S = v_p / v_u$ , i
- izlaznu otpornost,  $R_{iz}$ .

Poznato je:


$R_s = R_p = 500\Omega$ ,  $R = 100k\Omega$ ,  $V_U = 15V$  i  $V_T = 25mV$ .

Parametri tranzistora su:

$\beta = 100$ ,  $V_{BE} = 0.7V$ .


Parametri Zener diode su:

$V_{z0} = 6.2V$ ,  $r_z = 15\Omega$ .

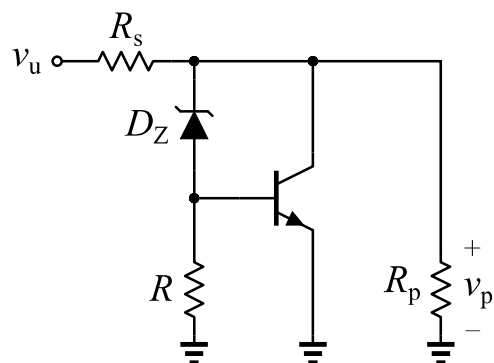

Sl. 4

a)

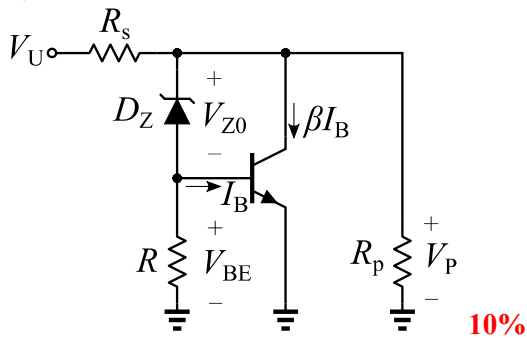

EQ1 :  $V_P \approx V_{Z0} + V_{BE} = 6.9V$

EQ2 :  $\frac{V_U - V_P}{R_s} = I_B + \frac{V_{BE}}{R} + \beta I_B + \frac{V_P}{R_P}$

$$I_B = \frac{1}{1 + \beta} \left( \frac{V_U}{R_s} - \frac{V_{BE}}{R} - \frac{V_P}{R_s || R_p} \right) = 23.693 \mu A$$


$$I_C = \beta I_B = 2.369 mA$$

$$g_m = \frac{I_C}{V_T} = 94.772 mS$$

$$r_\pi = \frac{\beta}{g_m} = \frac{V_T}{I_B} = 1.055 k\Omega$$

20%

b)

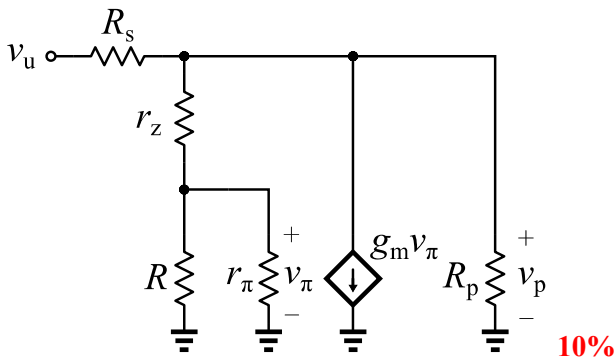


EQ1 :  $\frac{v_u - v_p}{R_s} = \frac{v_p - v_\pi}{r_z} + \frac{v_p}{R_p} + g_m v_\pi$

EQ2 :  $\frac{v_p - v_\pi}{r_z} = \frac{v_\pi}{R || r_\pi}$

$$S = \frac{v_p}{v_u} = \frac{1}{1 + R_s \left( \frac{1}{R_p} + \frac{1 + g_m (r_\pi || R)}{r_z + r_\pi || R} \right)} = 2.033 \times 10^{-2} V/V$$

30%

c)

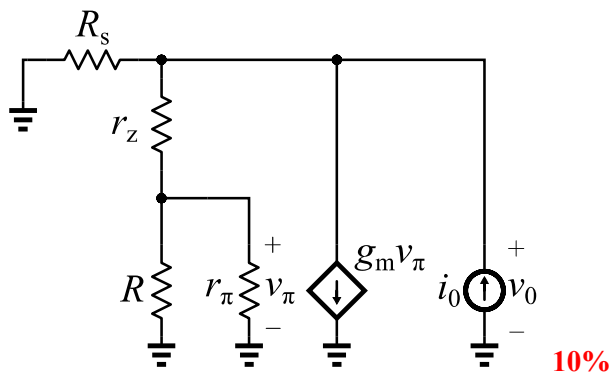

$$EQ1 : i_0 = g_m v_\pi + v_0 \frac{1}{R_s \parallel (r_z + R \parallel r_\pi)}$$

$$EQ2 : \frac{v_0 - v_\pi}{r_z} = \frac{v_\pi}{R \parallel r_\pi}$$

$$R_{iz} = \frac{v_0}{i_0} = R_s \parallel \left( \frac{r_z + r_\pi \parallel R}{1 + g_m (r_\pi \parallel R)} \right) = 10.376 \Omega \quad 20\%$$