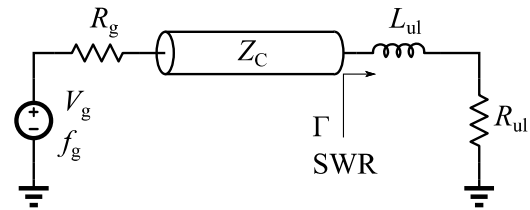




### RF Elektronika

1. Na slici 1 generator unutrašnje otpornosti  $R_g = 50\Omega$ , preko koaksijalnog kabla karakteristične impedanse  $Z_C = 50\Omega$ , napaja uređaj signalom frekvencije  $f_g = 5\text{GHz}$ . Ulaznu impedansu uređaja čine redna veza ulazne otpornost,  $R_{ul} = 25\Omega$ , i induktivnosti,  $L_{ul} = 5\text{nH}$ . Na ulazu uređaja naći:



Slika 1

- koeficijent refleksije  $\Gamma$  i
- koeficijent stojećeg talasa, SWR.

a)


$$X_{ul} = \omega_g L_{ul} = 2\pi f_g L_{ul} = 157.08\Omega, Z_{ul} = R_{ul} + jX_{ul} = 25 + j157.08\Omega \quad 25\%$$

$$\Gamma = \frac{Z_{ul} - Z_C}{Z_{ul} + Z_C} = 0.752 + j0.518 = 0.914 e^{j34.57^\circ}, |\Gamma| = 0.914 \quad 25\%$$

b)

$$SWR = \frac{1 + |\Gamma|}{1 - |\Gamma|} = 22.194 \quad 50\%$$

2. Na slici 2 je prikazan pojačavač klase C sa MOSFET tranzistorom. Zavisnost struje drejna od napona gejta-sors data je izrazom,  $I_d = I_{dss}(U_{gs} - V_T)^2$ , gde je  $I_{dss} = 0.5\text{A/V}^2$ , a napon praga  $V_T = 0.5\text{V}$ . Odrediti:

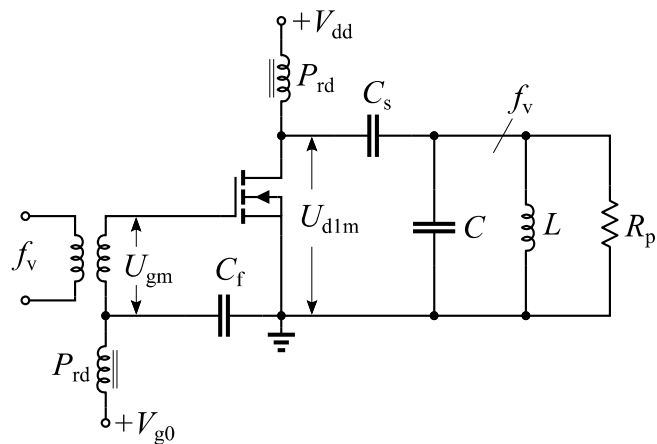

Slika 2

- napon polarizacije gejta  $V_{g0}$ , tako da pri visokofrekventnom pobudnom signalu napona amplitude  $U_{gm} = 1\text{V}$  ugao protoka struje drejna bude  $\theta_d = 50^\circ$  i

- korisnu sangu  $P_k$  na potrošaču  $R_p = 75\Omega$ .  
Poznato je:  $\alpha_1(50^\circ) = 0.3388$ .

a)

$$e_g(\theta) = V_{g0} + U_{gm} \cos(\theta) \Rightarrow e_g(\theta_d) = V_T, V_{g0} = V_T - U_{gm} \cos(\theta_d) = 0.353 \text{ V } 50\%$$

b)

$$\text{@ } \omega = \omega_v, R_{d0} \rightarrow \infty \Omega \Rightarrow R_d = R_{d0} \parallel R_p = R_p = 75\Omega$$

$$J_d = I_{dss} (V_{gs} - V_T)^2 = I_{dss} (e_g(\theta) - V_T)^2 \Rightarrow J_{d,max} = I_{dss} (e_g(0^\circ) - V_T)^2$$

$$J_{d,max} = I_{dss} (V_{g0} + U_{gm} - V_T)^2 = 363.674 \text{ mA } 20\%$$

$$J_{d1,max} = \alpha_1(\theta_d) J_{d,max} = 133.032 \text{ mA } 20\%$$

$$P_k = \frac{1}{2} J_{d1,max}^2 R_d = 663.657 \text{ mW } 10\%$$

3. Na slici 3 je prikazan AM modulator.


Odrediti:

a) amplitudu izlaznog napona  $U_{AM}$  u odsustvu modulatornog signala ( $u_n = 0V$ ) ako je amplituda nosioca  $U_v = 15mV$  a dinamička otpornost oscilatornog kola  $R_d = 10k\Omega$ .

b) stepn amplitudske modulacije  $m$  ako je amplituda modulatornog napona  $U_n = 0.5V$ .

Poznato je:  $R_b = 10k\Omega$ ,  $U_{be} = 0.7V$ ,

$V_{cc} = V_{ee} = 5V$  i  $V_T = 26mV$ .

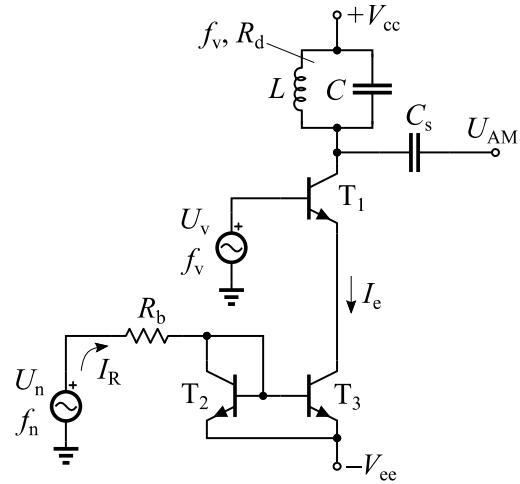

Slika 3

$$I_R = \frac{(u_n - V_{be} + V_{ee})}{R_b} = \frac{(V_{ee} - V_{be})}{R_b} \left( 1 + \frac{U_n}{V_{ee} - V_{be}} \cos(\omega_n t) \right)$$

$$I_R = I_{R0} (1 + m \cdot \cos(\omega_n t)), \quad I_{R0} = \frac{(V_{ee} - V_{be})}{R_b}, \quad m = \frac{U_n}{V_{ee} - V_{be}}$$

$$\beta \gg 1 \Rightarrow I_R \approx I_{c3} = I_{e1} \approx I_{c1} \Rightarrow g_{m1} = \frac{I_{c1}}{V_T} \approx \frac{I_R}{V_T}$$

$$u_{AM}(m) = g_{m1} u_v R_d \approx I_R R_d \frac{U_v}{V_T} \cos(\omega_v t) = I_{R0} R_d \frac{U_v}{V_T} (1 + m \cdot \cos(\omega_n t)) \cos(\omega_v t)$$

$$U_{AM} = u_{AM}(0) = I_{R0} R_d \frac{U_v}{V_T}$$

a)

$$I_{R0} = \frac{(V_{ee} - V_{be})}{R_b} = 430 \mu A \quad 25 \%$$

$$U_{AM} = I_{R0} R_d \frac{U_v}{V_T} = 2.481 V \quad 25 \%$$

b)

$$m = \frac{U_n}{V_{ee} - V_{be}} = 0.116 (11.6 \%) \quad 50 \%$$

4. PLL sintetizator sa slike 4 sastoji se od:

- kvarcnog oscilatora,  $f_Q = 4\text{MHz}$ ,
- pred-delitelja,  $R = 200$ ,
- preskalera,  $P = 80$ , i
- programirljivog delitelja ( $N_{\min} - N_{\max} = (500 - 1500)$ ).

Odrediti:

- a) korak (rezoluciju) u sintezi frekvencije,  $\Delta f$ , i
- b) opseg frekvencija ( $f_{0\min} - f_{0\max}$ ) u kome PLL sintetiše frekvencije.


a)

$$\Delta f_0 = f_q \frac{P}{R} = 1.6 \text{ MHz } 50\%$$

b)

$$f_{0,\min} = N_{\min} \Delta f_0 = 800 \text{ MHz } 25\%$$

$$f_{0,\max} = N_{\max} \Delta f_0 = 2.4 \text{ GHz } 25\%$$

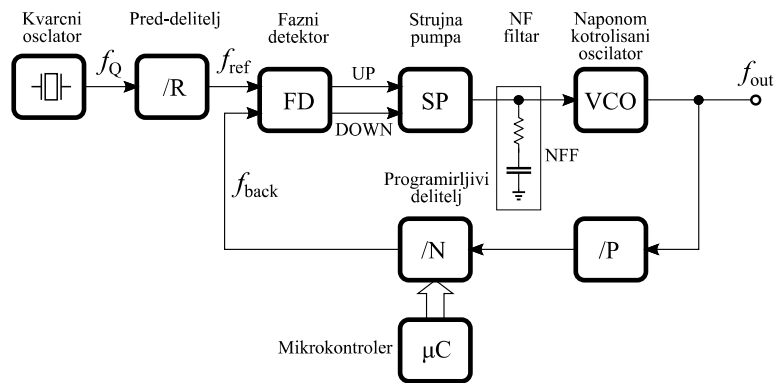

Slika 4