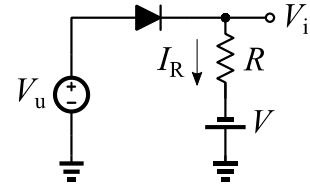


**OSNOVI ELEKTRONIKE****Zadaci****1.** Za diodno kolo sa Sl. 1 odrediti i nacrtati zavisnost:a) izlaznog napona, V_i , ib) struje, I_R , u funkciji ulaznog napona V_u .

Poznato je:

 $R_1=1k\Omega$, $V=2V$, $-5V \leq V_u \leq 5V$.


Parametri modela diode su:

 $V_{D0}=0.6V$, $r_d=0\Omega$.


Sl. 1

Za $V_u \geq V_{D0} - V = -1.4V$ dioda vodi. **20%**a) **20%**

$$V_i = \begin{cases} -2V, & V_u < -1.4V \\ V_u - 0.6V, & V_u \geq -1.4V \end{cases}$$

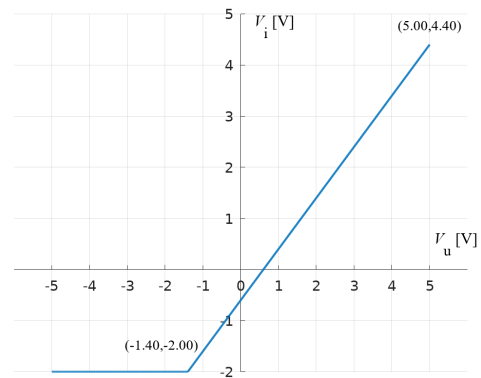**20%**b) **20%**

$$I_R = \begin{cases} 0A, & V_u < -1.4V \\ 1mS \cdot V_u + 1.4mA, & V_u \geq -1.4V \end{cases}$$

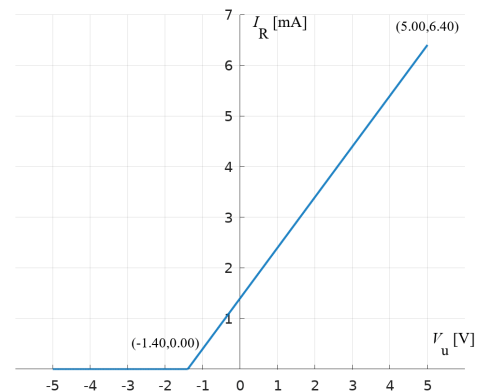**20%**

2. Za pojačavač sa Sl. 2 odrediti:

- jednosmerni napon na sorsu tranzistora, M2,
- parametre modela za male signle, g_m , r_o , i
- naponsko pojačanje, $A_n = V_i/V_u$.

Poznato je:


$$R_D = 20k\Omega, R_p = 10k\Omega, V_{DD} = 3.3V, V_U = 0.6V, V_G = 1.3V.$$

Parametri tranzistora su:

$$A_1 = 2.5mA/V^2, A_2 = 6.25mA/V^2,$$

$$V_{A1} = V_{A2} = 80V, V_{TH1} = V_{TH2} = 0.4V.$$

Smatrati da je kapacitivnost spreznog kondnezatora, C_S , izuzetno velika.

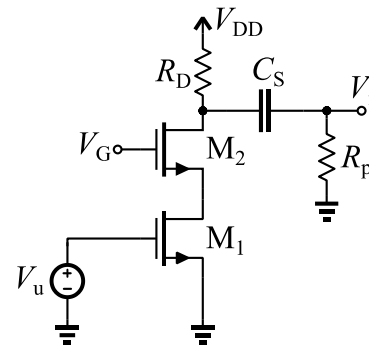


Sl. 2

a)

$$I_{D1} = A_1(V_{GS1} - V_{TH1})^2 = 100\mu A = I_{D2} \Rightarrow$$

$$V_{GS2} = V_{TH2} + \sqrt{\frac{I_{D2}}{A_2}} = 0.526V, \text{ 15\%}$$
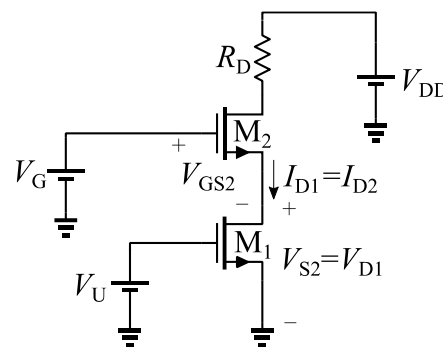
$$V_{S2} = V_{D1} = V_G - V_{GS2} = 0.774V \text{ 15\%}$$



b)

$$g_{m1} = \frac{2I_{D1}}{V_{GS1} - V_{TH1}} = 1mS, r_{o1} = \frac{V_{A1}}{I_{D1}} = 800k\Omega \text{ 10\%}$$

$$g_{m1} = \frac{2I_{D2}}{V_{GS2} - V_{TH2}} = 1.581mS, r_{o2} = \frac{V_{A1}}{I_{D1}} = 800k\Omega \text{ 10\%}$$


c)

$$\mu_1 = g_{m1}r_{o1} = 800, \mu_2 = g_{m2}r_{o2} = 1265$$

$$R_L = R_D || R_p = 6.667k\Omega \text{ 20\% 10\%}$$

$$R_{S2} = \frac{R_L + r_{o2}}{1 + \mu_2} = 636.7\Omega \text{ 10\%}$$
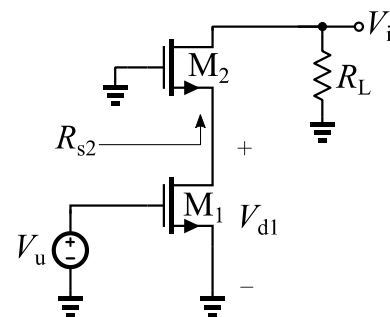
$$A_n = \frac{V_i}{V_u} = \frac{V_i}{V_{d1}} \cdot \frac{V_{d1}}{V_u} = \frac{(1 + \mu_2)R_L}{R_L + r_{o2}} \cdot \frac{-\mu_1 R_{S2}}{R_{S2} + r_{o1}} = -10.533 \text{ 20\%}$$



10%

3. Za filter sa Sl. 3 odrediti:

a) prenosnu funkciju, $T(s) = V_i/V_u$,

b) polove funkcije prenosa i


c) tip filtra.

Poznato je:

$R_1=R_2=10k\Omega$, $C_1=C_2=1nF$.

Operacioni pojačavač ima sledeće karakteristike:

$A \rightarrow \infty V/V$, $R_{ul} \rightarrow \infty\Omega$, $R_{iz} \rightarrow 0\Omega$.

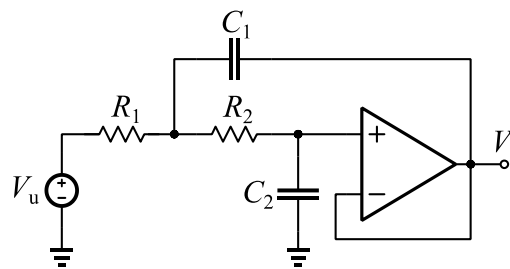


Sl. 3

a)

$$V_2 = V_i$$
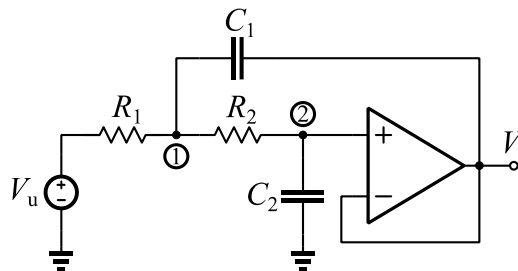
$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} + sC_1 & -sC_1 - \frac{1}{R_2} \\ -\frac{1}{R_2} & \frac{1}{R_2} + sC_2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_i \end{bmatrix} = \begin{bmatrix} V_u \\ 0 \end{bmatrix} \quad 30\%$$



$$\Delta = \frac{1}{R_1 R_2} + sC_2 \left(\frac{1}{R_1} + \frac{1}{R_2} + sC_1 \right) \quad 10\%$$

$$\Delta_{V_i} = \frac{V_u}{R_1 R_2} \quad 10\%$$

$$T(s) = \frac{V_i}{V_u} = \frac{\Delta_{V_i}}{\Delta} \cdot \frac{1}{V_u} = \frac{1}{1 + sC_2(R_1 + R_2) + s^2 R_1 R_2 C_1 C_2} \quad 10\%$$

b)

$$R_1 = R_2 = R, C_1 = C_2 = C, \tau = RC = 10\mu s$$

$$T(s) = \frac{D(s)}{N(s)} \Rightarrow N(s) = 1 + sC_2(R_1 + R_2) + s^2 R_1 R_2 C_1 C_2 = 1 + s(2\tau) + s^2 \tau^2 = 0$$

$$s_{1,2} = -\frac{1}{\tau} = -10^5 \text{ rad/s} \quad 20\%$$

c) Propusnik niskih frekvencija (low pass). 20%

4. Za oscilator sa Sl. 4 odrediti:

- frekvenciju oscilovanja i
- otpornost baze za mali signal, r_π , pri kojoj je ispunjen uslov oscilovanja.


Poznato je:

$R_1=400k\Omega$, $R_2=100\Omega$, $C_1=400nF$, $C_2=200nF$, $L=500nH$,
 $V_{CC}=3.3V$.

Tranzistor ima sledeće karakteristike:

$\beta = 80$, $V_T=kT/q \approx 25mV$.

Smatrati da kapacitivnost C_S ima izuzetno veliku vrednost.

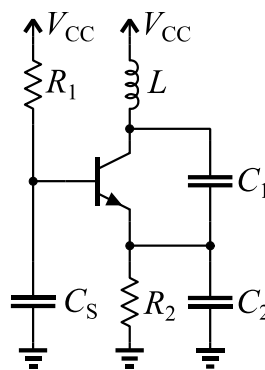

Sl. 4

$$v_\pi = v_b - v_e = -v_e \quad (10\%)$$

$$\begin{bmatrix} \frac{1}{R_2} + \frac{1+\beta}{r_\pi} + s(C_1 + C_2) & -sC_1 \\ -\frac{\beta}{r_\pi} - sC_1 & \frac{1}{sL} + sC_1 \end{bmatrix} \begin{bmatrix} v_e \\ v_c \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix} \quad (20\%)$$

$$\Delta = \frac{1}{L} \left(\frac{1}{R_2} + \frac{1+\beta}{r_\pi} \right) + s \frac{(C_1 + C_2)}{L} + s^2 C_1 \left(\frac{1}{R_2} + \frac{1}{r_\pi} \right) + s^3 C_1 C_2 \quad (20\%)$$


a) 20%

$$Im\{\Delta\} = \omega_0 \frac{(C_1 + C_2)}{L} - \omega_0^3 C_1 C_2 \Rightarrow C_{ek} = \frac{C_1 C_2}{C_1 + C_2} = 133.33nF, \omega_0 = \frac{1}{\sqrt{L C_{ek}}} = 3.873 \cdot 10^6 rad/s$$

$$f_o = \frac{\omega_0}{2\pi} = 616.40kHz$$

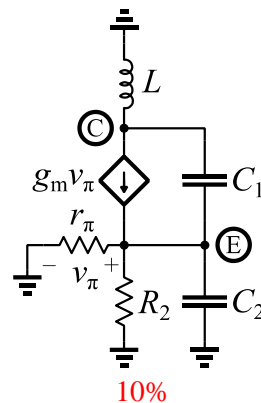b) 20%

$$Re\{\Delta\} = \frac{1}{L} \left(\frac{1}{R_2} + \frac{1+\beta}{r_\pi} \right) - \omega_0^2 C_1 \left(\frac{1}{R_2} + \frac{1}{r_\pi} \right) \Rightarrow r_\pi = R_2 \left(\beta \frac{C_1}{C_2} - 1 \right) = 3.9k\Omega$$



10%