



OSNOVI ELEKTRONIKE

Zadaci

1. Za diodno kolo sa Sl. 1 odrediti i nacrtati zavisnost:


- a) Izlaznog napona, V_i , i
- b) Struje I_u , u funkciji ulaznog napona V_u .

Poznato je:


$R_1 = R_2 = 1k\Omega$ i $-10V \leq V_u \leq 10V$.

Parametri modela dioda su:

$V_{D0} = 0.7V$, $r_d = 0\Omega$, $V_{Z0} = 3.3V$ i $r_z = 0\Omega$.

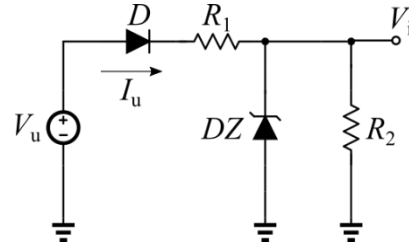


Sl. 1

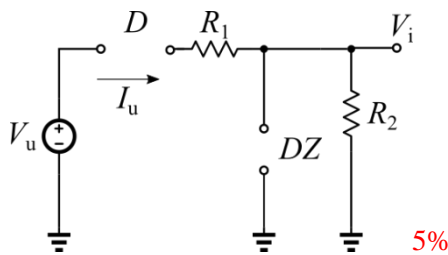

Za $-10V \leq V_u \leq 0.7V$ diode D i DZ ne vode: **5%**

$$V_i = 0V \quad \mathbf{5\%}$$


$$I_u = 0mA \quad \mathbf{5\%}$$

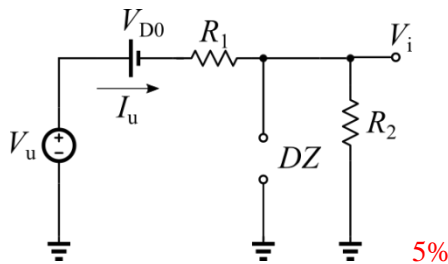

Za $0.7V < V_u \leq 7.3V$ dioda D vodi i dioda DZ ne vodi: **5%**

$$V_i = \frac{R_2}{R_1 + R_2} (V_u - V_{D0}) = \frac{1}{2} V_u - 0.35 [V] \quad \mathbf{5\%}$$

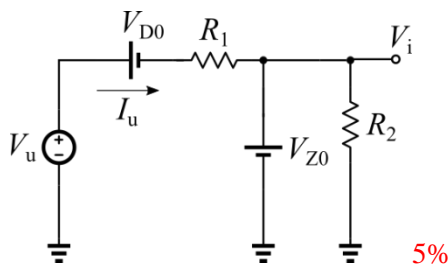
$$I_u = \frac{V_u - V_{D0} - V_i}{R_1} = \frac{1}{2} V_u - 0.35 [mA] \quad \mathbf{5\%}$$




Za $7.3V < V_u \leq 10V$ dioda D vodi i dioda DZ vodi inverzno: **5%**

$$V_i = V_{Z0} = 3.3V \quad \mathbf{5\%}$$
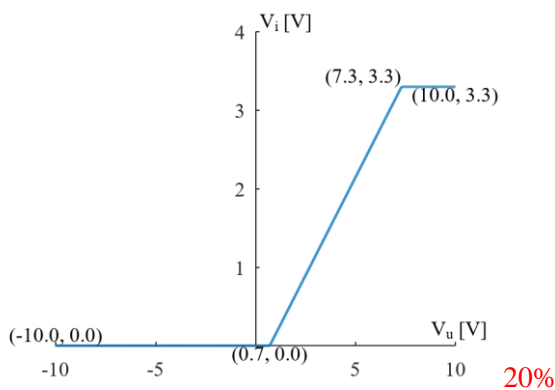
$$I_u = \frac{V_u - V_{D0} - V_i}{R_1} = V_u - 4 [mA] \quad \mathbf{5\%}$$



20%

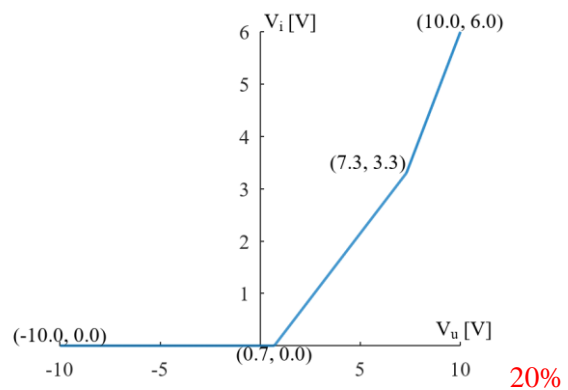

20%

2. Za pojačavač sa Sl. 2 odrediti:

- Parametre modela za male signale, g_m i r_0 ,
- Naponsko pojačanje, $A_n = v_p/v_u$ i
- Izlaznu otpornost, R_{iz} .


Poznato je:

$R_1=100k\Omega$, $R_2=400k\Omega$, $R_3=1.5k\Omega$, $R_u=100\Omega$,
 $R_p=5k\Omega$ i $V_{DD}=5V$.

Parametri tranzistora su:


$A = 8mA/V^2$, $V_{TH}=0.5V$ i $V_A=100V$.

Smatrati da su kapacitivnosti sprežnih kondenzatora, C_S , izuzetno velike.

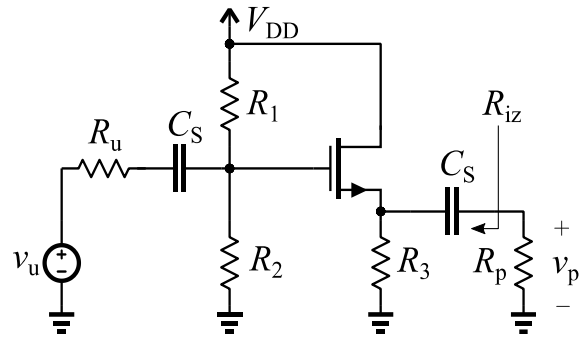

Sl. 2

a)

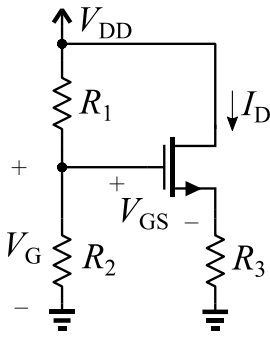

10%

$$V_G = V_{GS} + I_D R_3$$

$$V_G - V_{TH} = V_{GS} - V_{TH} + A (V_{GS} - V_{TH})^2 R_3$$


$$V_{ov} = V_{GS} - V_{TH}$$

$$A R_3 V_{ov}^2 + V_{ov} - (V_G - V_{TH}) = 0$$

$$V_{ov} = 0.5V \Rightarrow I_D = A V_{ov}^2 = 2mA \quad 10\%$$

$$g_m = 2A V_{ov} = 8mS, \quad r_0 = \frac{V_A}{I_D} = 50k\Omega \quad 10\%$$

b)

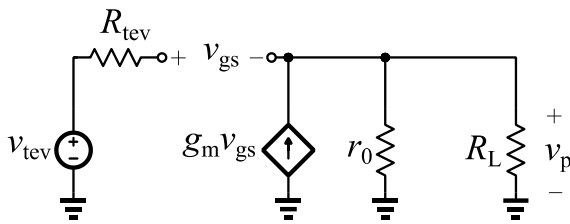

$$R_g = R_1 || R_2 = 80k\Omega$$

$$R_{tev} = R_g || R_u = 99.875\Omega$$

$$v_{tev} = \frac{R_g}{R_g + R_u} v_u = 0.9988 v_u$$


$$R_L = R_3 || R_p = 1.154k\Omega$$

EQ1 : $v_{gs} = v_{tev} - v_p$

EQ2 : $v_p \frac{1}{R_L || r_0} - g_m v_{gs} = 0 \quad 10\% \quad 20\%$

$$A_n = \frac{v_p}{v_{tev}} \times \frac{v_{tev}}{v_u} = \frac{g_m (R_L || r_0)}{1 + g_m (R_L || r_0)} \times \frac{R_g}{R_g + R_u} = 0.899V/V \quad 10\%$$

c)

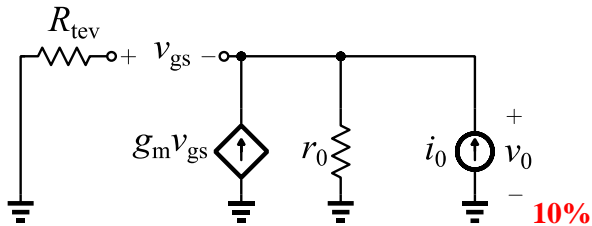

$$EQ1 : v_{gs} = -v_0$$

$$EQ1 : -i_0 - g_m v_{gs} + v_0 \frac{1}{r_0} = 0$$

$$R_T = \frac{v_0}{i_0} = \frac{r_0}{1 + \mu} = 124.69 \Omega$$

$$R_{iz} = R_T || R_3 = 115.119 \Omega \quad 20\%$$


3. Za filtersko kolo sa Sl. 3 odrediti:

- Prenosnu funkciju $H_A(s) = V_A/V_u$ i njen tip,
- Prenosnu funkciju $H_B(s) = V_B/V_u$ i njen tip,
- Prenosnu funkciju $H_C(s) = V_C/V_u$,
- Pojačanja funkcije $H_C(s)$ na niskim i visokim učestanostima.


Poznato je:

$R = 10k\Omega$, $C_1 = 100pF$ i $C_2 = 10nF$.

Operacioni pojačavači su idealni.

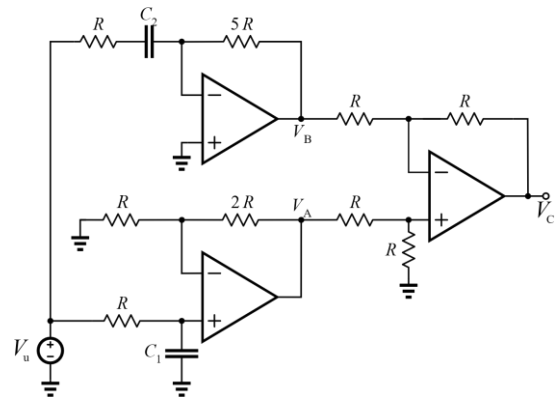

Sl. 3

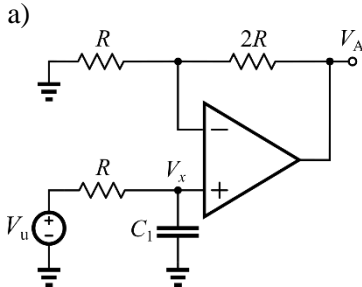


$$V_x = \frac{\frac{1}{sC_1}}{\frac{1}{sC_1} + R} V_u = \frac{1}{1 + sRC_1} V_u$$

$$V_A = \left(1 + \frac{2R}{R}\right) V_x = 3V_x = \frac{3}{1 + sR_1C_1} V_u$$

$$H_A(s) = \frac{3}{1 + sRC_1}$$

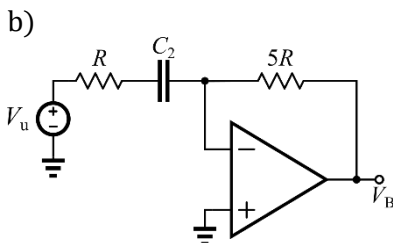$H_A(s)$ - Propusnik niskih učestanosti (25 %)



$$V_B = -\frac{5R}{R + \frac{1}{sC_2}} V_u = -5 \frac{sRC_2}{1 + sRC_2} V_u$$


$$H_B(s) = -5 \frac{sRC_2}{1 + sRC_2}$$

$H_B(s)$ - Propusnik visokih učestanosti (20 %)

c)

Kolo za oduzimanje (diferencijalni pojačavač): (25 %)
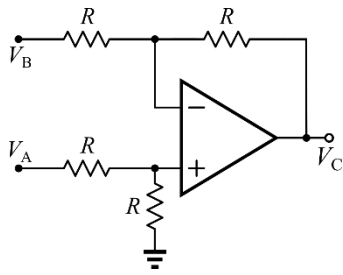
$$\begin{aligned} V_C &= \frac{R}{R+R} \left(1 + \frac{R}{R}\right) V_A - \frac{R}{R} V_B = V_A - V_B \\ &= \left(\frac{3}{1 + sRC_1} + \frac{5sRC_2}{1 + sRC_2}\right) V_u \\ &= \frac{3(1 + sRC_2) + 5sRC_2(1 + sRC_1)}{(1 + sRC_1)(1 + sRC_2)} V_u \end{aligned}$$



$$H_C(s) = \frac{5s^2R^2C_1C_2 + 8sRC_2 + 3}{s^2R^2C_1C_2 + sR(C_1 + C_2) + 1}$$

d)

Na niskim učestanostima: $A_0 = H_C(s \rightarrow 0) = 3$ (15 %)

Na visokim učestanostima: $A_\infty = H_C(s \rightarrow \infty)$: (15 %)

$$A_\infty = \lim_{s \rightarrow \infty} \frac{5s^2R^2C_1C_2 + 8sRC_2 + 3}{s^2R^2C_1C_2 + sR(C_1 + C_2) + 1} = \lim_{s \rightarrow \infty} \frac{s^2 \left(5R^2C_1C_2 + \frac{8RC_2}{s} + \frac{3}{s^2} \right)}{s^2 \left(R^2C_1C_2 + \frac{R(C_1 + C_2)}{s} + \frac{1}{s^2} \right)} = 5$$

4. Za regulator sa Sl. 4 odrediti:

a) Jednosmernu vrednost izlaznog napona, V_P ,

b) Parametre modela za male signale, g_m i r_π , i

c) Osetljivost regulatora, $S = v_p/v_u$.

Poznato je:


$R_s = R_p = 500\Omega$, $R = 100k\Omega$, $V_U = 15V$ i $V_T = 25mV$.

Parametri tranzistora su:

$\beta = 100$ i $V_{BE} = 0.7V$.


Parametri Zener diode su:

$V_{Z0} = 6.2V$ i $r_z = 15\Omega$.

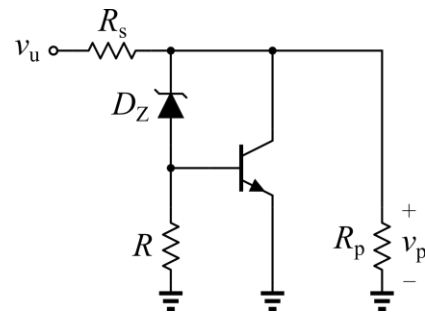

Sl. 4

a) i b)

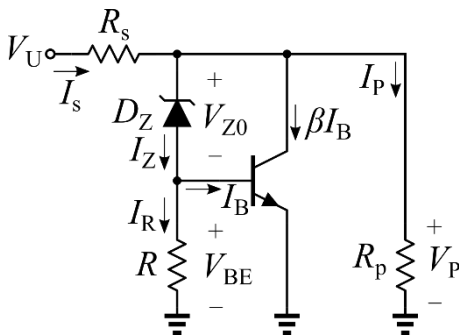

$$EQ1: V_P \approx V_{Z0} + V_{BE} = 6.9V$$

$$EQ2: \frac{V_U - V_P}{R_s} = I_B + \frac{V_{BE}}{R} + \beta I_B + \frac{V_P}{R_p}$$

$$I_B = \frac{1}{1 + \beta} \left(\frac{V_U}{R_s} - \frac{V_{BE}}{R} - \frac{V_P}{R_s || R_p} \right) = 23.693$$

$$I_C = \beta I_B = 2.369mA$$

$$g_m = \frac{I_C}{V_T} = 94.772mS$$

$$r_\pi = \frac{\beta}{g_m} = \frac{V_T}{I_B} = 1.055k\Omega$$


Izraz za V_P - 15 %

Šema za DC - 10 %

Izraz za I_B - 15 %

Parametri - 5 % + 5 %

c)

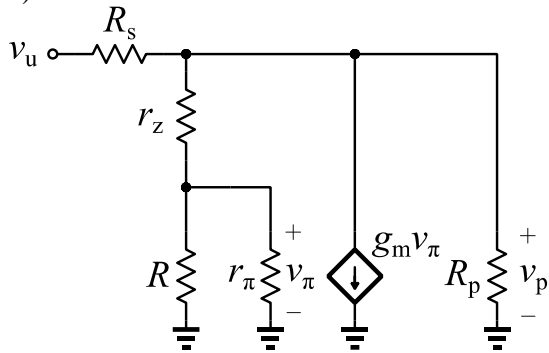

$$EQ1: \frac{v_u - v_p}{R_s} = \frac{v_p - v_\pi}{r_z} + \frac{v_p}{R_p} + g_m v_\pi$$

$$EQ2: \frac{v_p - v_\pi}{r_z} = \frac{v_\pi}{R || r_\pi}$$

$$S = \frac{v_p}{v_u} = \frac{1}{1 + R_s \left(\frac{1}{R_p} + \frac{1 + g_m(r_\pi || R)}{r_z + r_\pi || R} \right)} = 2.033 \times 10^{-2} V/V$$

Šema za AC – 10 %

Jednačine – 10 % + 10 %

Izraz za osetljivost – 20 %