



OSNOVI ELEKTRONIKE

Zadaci

1. Za diodno kolo sa Sl. 1 odrediti i nacrtati zavisnost:


- a) Izlaznog napona,  $V_i$ , i
- b) Struje  $I_{R3}$ , u funkciji ulaznog napona,  $V_u$ .

Poznato je:

$R_1=R_2=R_3=1k\Omega$ ,  $V_1=3V$  i  $-10V \leq V_u \leq 10V$ .

Parametri modela diode su:


$V_{D0}=0.6V$ ,  $r_d=0\Omega$ .

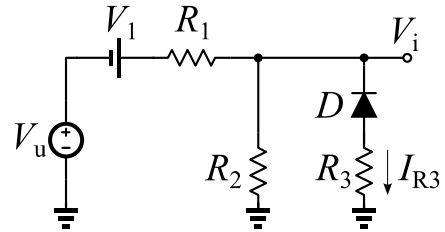

Sl. 1

Uslov da dioda vodi je:  $\frac{R_2}{R_1+R_2}(V_u + V_1) \leq -V_{D0}$ . **10%**

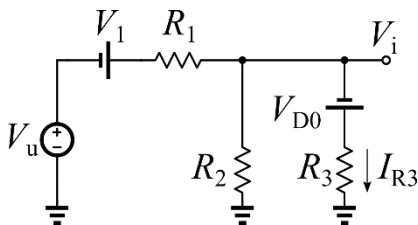Iz uslova se dobija da dioda vodi za  $-10V \leq V_u \leq -4.2V$  i tada važi:




5%

$$V_i = \frac{R_2 || R_3}{R_2 || R_3 + R_1}(V_u + V_1) - \frac{R_1 || R_2}{R_1 || R_2 + R_3}V_{D0} = \frac{1}{3}V_u + 0.8 [V] \quad \mathbf{10\%}$$

$$I_{R3} = \frac{V_i + V_{D0}}{R_3} = \frac{1}{3}V_u + 1.4 [mA] \quad \mathbf{10\%}$$

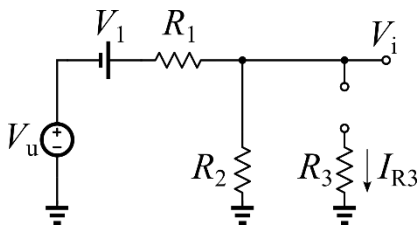
Dioda ne vodi za  $-4.2V < V_u \leq 10V$  i tada važi:




5%

$$V_i = \frac{R_2}{R_1 + R_2}(V_u + V_1) = \frac{1}{2}V_u + 1.5 [V] \quad \mathbf{10\%}$$

$$I_{R3} = 0 [mA] \quad \mathbf{10\%}$$

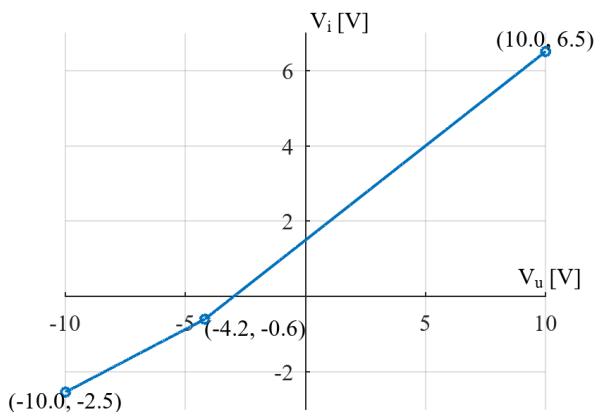

20%

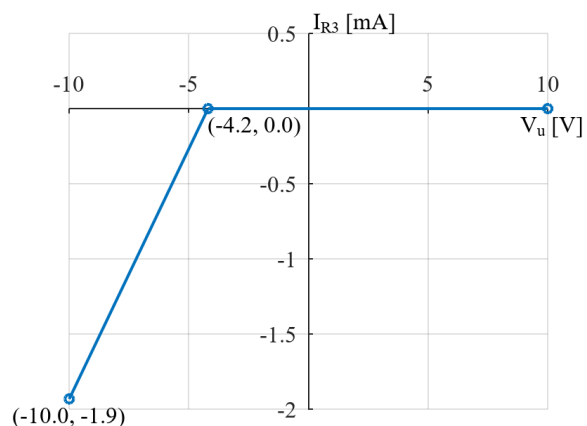

20%

2. Za pojačavač sa Sl. 2 odrediti:

- parametre modela za male signale,  $g_m$  i  $r_\pi$ ,
- naponsko pojačanje,  $A_n = v_p/v_u$  i
- ulaznu otpornost,  $R_{ul}$ .


Poznato je:

$R_1=50k\Omega$ ,  $R_2=140k\Omega$ ,  $R_3=1k\Omega$ ,  $R_u=50\Omega$ ,  $R_p=1k\Omega$ ,  
 $V_{CC}=10V$ .

Parametri tranzistora su:

$\beta = 100$ ,  $V_{BE} = 0.6V$ ,  $V_A \rightarrow \infty V$ .

Smatrati da su kapacitivnosti sprežnih kondenzatora,  $C_S$ , izuzetno velike.

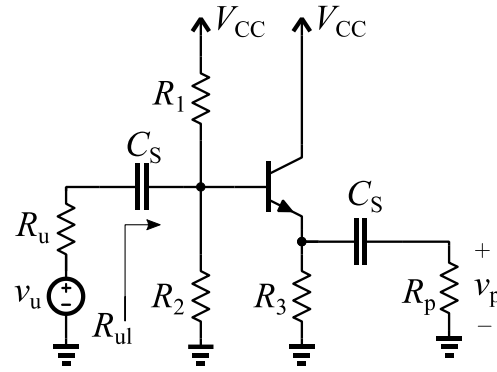


Sl. 2

a)

$$V_{BB} = V_{CC} \cdot \frac{R_2}{R_2 + R_1} = 7.368V, R_{BB} = R_1 || R_2 = 36.842k\Omega \quad \mathbf{10\%}$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_{BB} + (1 + \beta)R_3} = 49.103\mu A, I_C = \beta I_B = 4.910mA \quad \mathbf{10\%}$$
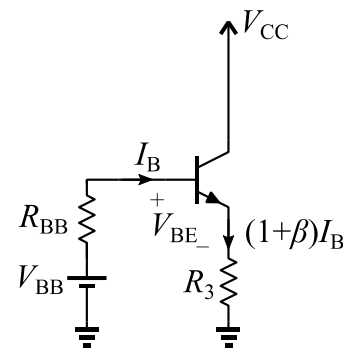
$$g_m = \frac{I_C}{V_T} = 196.411mS, r_\pi = 509.137\Omega \quad \mathbf{10\%}$$




**10%**

b)

$$v_{tev} = \frac{R_{BB}}{R_{BB} + R_u} v_u, R_{tev} = R_{BB} || R_u = 49.932\Omega \quad \mathbf{10\%}$$

$$R_L = R_3 || R_p = 500\Omega, R_b = r_\pi + (1 + \beta)R_L = 51.01k\Omega \quad \mathbf{10\%}$$
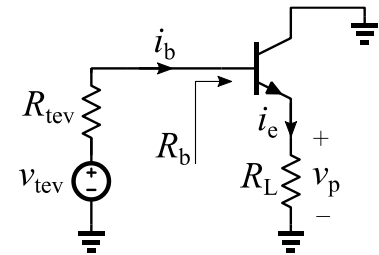
$$A_n = \frac{v_p}{v_u} = \frac{v_p}{i_e} \cdot \frac{i_e}{i_b} \cdot \frac{i_b}{v_{tev}} \cdot \frac{v_{tev}}{v_u} = R_L \cdot (1 + \beta) \cdot \frac{1}{R_{tev} + R_b} \cdot \frac{R_{BB}}{R_{BB} + R_u} = 0.988 \quad \mathbf{10\%}$$



**10%**

c)

$$R_{ul} = R_{BB} || R_b = 21.392 k\Omega \quad \mathbf{20\%}$$


**3.** Za kolo filtra sa Sl. 3 odrediti:

- a) prenosnu funkciju,  $T(s)=V_i/V_u$ ,
- b) polove prenosne funkcije i
- c) tip filtra.

Poznato je:

$$R_1=R_2=10\text{k}\Omega \text{ i } C_1=C_2=100\text{nF}.$$

Operacioni pojačavač je idealan.

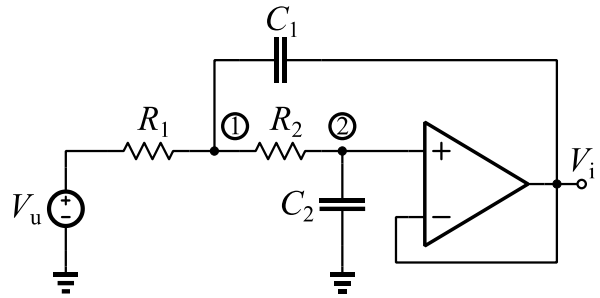

a)

10%  $v_i = v_2$

20% 
$$\begin{bmatrix} G_1 + G_2 + sC_1 & -G_2 - sC_2 \\ -G_2 & G_2 + sC_2 \end{bmatrix} \begin{bmatrix} v_1 \\ v_i \end{bmatrix} = \begin{bmatrix} G_1 v_u \\ 0 \end{bmatrix}$$

40% 
$$H(s) = \frac{v_i}{v_u} = \frac{1}{1 + C_2(R_1 + R_2)s + s^2 C_1 C_2 R_1 R_2} = \frac{N(s)}{D(s)}$$

b)

20% 
$$D(s) = 1 + 2 \cdot 10^{-3}s + 10^{-6}s^2 = 0 \Rightarrow s_1 = s_2 = -10^3 \frac{\text{rad}}{\text{s}}$$

c)

10% NF (LP) filter

4. Za regulator sa Sl. 4 odrediti:

- a) jednosmerni napon na gejtu tranzistora,  $V_G$
- b) parametre za male signale,  $g_m$  i  $r_o$ , i
- c) izlaznu otpornost  $R_o$ .

Poznato je:

$R_1=10\text{k}\Omega$ ,  $R_2=15\text{k}\Omega$ ,  $V_{REF}=1\text{V}$  i  $V_{DD}=3.3\text{V}$ .


Tranzistor ima sledeće parametre:

$V_{TH}=0.35\text{V}$ ,  $A=1.6\text{mA/V}^2$ ,  $V_A=50\text{V}$ .

Operacioni pojačavač ima sledeće parametre:

$A_0=10^3\text{ V/V}$ ,  $R_{ul} \rightarrow \infty\Omega$ ,  $R_{iz} \rightarrow 0\Omega$ .

Za jednosmerni režim smatrati da  $A_0 \rightarrow \infty\text{ V/V}$ .

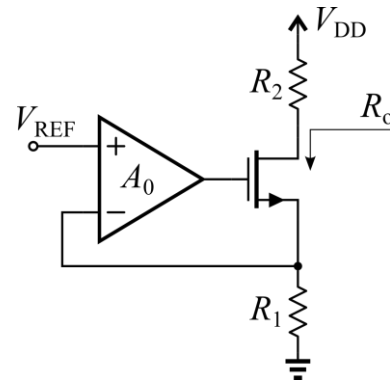

Sl. 4

a)

(10%)  $V_S = V_{REF} = 1\text{V}$

(10%)  $I_D = \frac{V_S}{R_1} = 100\mu\text{A}$

(10%)  $V_{ov} = \sqrt{\frac{I_D}{A}} = 250\text{mV}$

(5%)  $g_m = 2AV_{ov} = 800\mu\text{S}$


(5%)  $r_o = \frac{V_A}{I_D} = 500\text{k}\Omega$

b)

(5%)  $V_{GS} = V_{TH} + V_{ov} = 0.6\text{V}$

(5%)  $V_G = V_{GS} + V_S = 1.6\text{V}$

c)

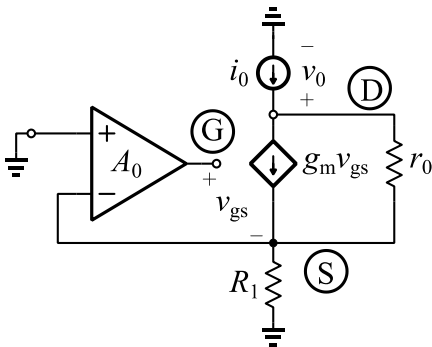

(10%)  $i_0 = \frac{v_0 - v_s}{r_o} + g_m v_{gs}$

(10%)  $i_0 = \frac{v_s}{R_1}$

(10%)  $v_g = -A_0 v_s$

---

(10%)  $R_o = r_o + (1 + g_m r_o (1 + A_0)) R_1 = 4.005\text{G}\Omega$

10%