

OSNOVI ELEKTRONIKE
Modul elektroenergetika (3OEP3A01, 2OEP3O03)

- Studenti koji su položili zadatke na prvom kolokvijumu imaju mogućnost da rade samo drugu polovinu pismenog ispita (3 i 4 zadatak) ukoliko su zadovoljni rezultatima sa prvog kolokvijuma.

1. Zadatak

Za kolo pojačavača sa slike 1 odrediti:

- Jednosmerni napon na emitoru tranzistora, V_E ;
- Izlaznu otpornost R_{iz} .
- Naponsko pojačanje $A_n = \frac{v_{iz}}{v_g}$


Parametri tranzistora su: $V_{BE} = 0,7 V$

$h_{21E} = \beta = 100$; $h_{22E} = 0 S$

($r_o \rightarrow \infty$). Poznato su elementi kola:

$R_B = 40 k\Omega$; $R_p = 1 k\Omega$; $R_g = 1 k\Omega$;

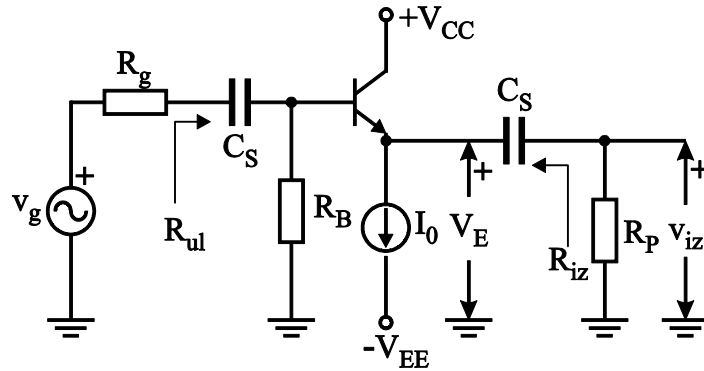$I_0 = 5 mA$; $V_{CC} = V_{EE} = 10 V$; $C_S \rightarrow \infty$.




Rešenje:

a)

$$R_B I_B + V_{BE} = V_E$$


$$I_o = I_E = (1 + \beta) I_B$$
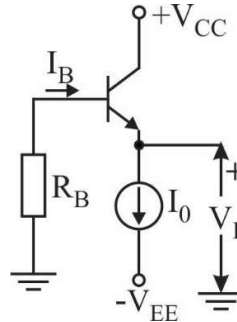
$$V_E = -V_{BE} - \frac{I_o R_B}{1 + \beta} = -2,7 V$$



$$h_{11} = \frac{V_T}{I_B} = \frac{V_T}{I_C} \beta = 520 \Omega$$

b)

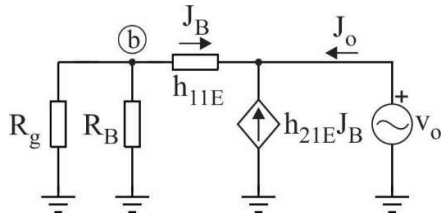


$$\frac{v_b}{R_B} + \frac{v_b}{R_g} + i_b = 0$$

$$i_b + h_{21E} \cdot i_b + i_o = 0$$

$$i_b = \frac{v_b - v_o}{h_{11E}}$$

$$R_{iz} = \frac{v_o}{i_o} = \frac{h_{11E} + R_g \parallel R_B}{(1 + h_{21E})} = 14,6 \Omega$$

c)

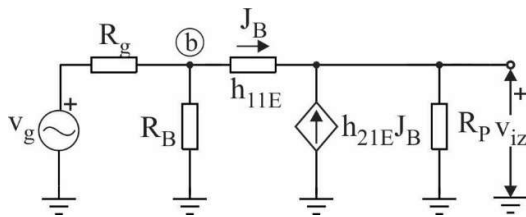

$$\frac{v_b}{R_B} + i_b + \frac{v_b - v_g}{R_g} = 0$$

$$\frac{v_{iz}}{R_p} - h_{21E} \cdot i_b - i_b = 0$$

$$i_b = \frac{v_b - v_{iz}}{h_{11E}}$$

$$i_b = \frac{R_B}{h_{11E}(R_B + R_g) + R_B R_g} v_g - \frac{(R_B + R_g)}{h_{11E}(R_B + R_g) + R_B R_g} v_{iz}$$


$$v_{iz} = (1 + h_{21E}) i_b R_p$$

$$A_n = \frac{v_{iz}}{v_g} = \frac{R_B R_p (1 + h_{21E})}{h_{11E}(R_B + R_g) + R_B R_g + (1 + h_{21E}) R_p (R_B + R_g)} = 0,96$$

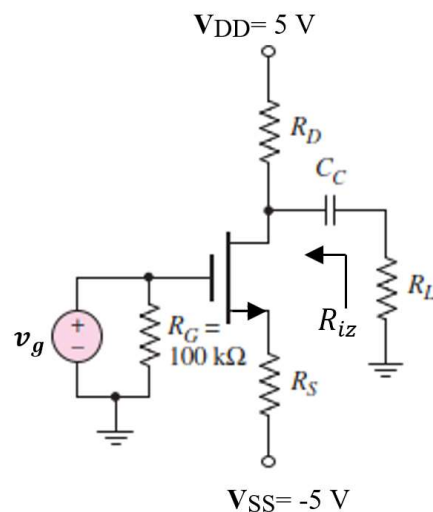2. Zadatak

Parametri tranzistora u kolu sa slike su $A = 0,5 \text{ mA/V}^2$ i $V_t = 2,5 \text{ V}$, $\lambda = 0,01 \text{ V}^{-1}$. Elementi kola su: $R_S = 250 \Omega$; $R_D = 2 \text{ k}\Omega$; $R_L = 6 \text{ k}\Omega$. Odrediti:

- Radnu tačku tranzistora i dinamičke parametre tranzistora.
- Naponsko pojačanje $A_n = v_{iz}/v_g$.
- Izlaznu otpornost tranzistora R_{iz} .



Rešenje:

$$V_S = R_S \cdot I_D + V_{SS}$$

$$V_{GS} = -V_S = -V_{SS} - R_S \cdot I_D$$

$$I_D = A \cdot (V_{GS} - V_t)^2$$

$$V_{GS} - V_t + V_t = -R_S \cdot A \cdot (V_{GS} - V_t)^2 - V_{SS}$$

$$R_S \cdot A \cdot V_x^2 + V_x + V_{SS} + V_t = 0$$

$$0,125 \cdot V_x^2 + V_x - 2,5 = 0$$

$$V_x = \frac{-1 \pm \sqrt{1 + 4 \cdot 2,5 \cdot 0,125}}{0,25}$$

$$V_{x1} = -10 \text{ V}$$

$$V_{x2} = 2 \text{ V}$$

$$I_D = A \cdot V_x^2 = 2 \text{ mA}$$

$$g_m = 2 \cdot \sqrt{A \cdot I_D} = 2 \text{ mS}$$

$$r_o = \frac{1}{\lambda \cdot I_D} = 50 \text{ k}\Omega$$

$$\mu = r_o \cdot g_m = 100$$

$$V_D = V_{DD} - R_D I_D = 1 \text{ V}$$

$$V_S = R_S I_S + V_{SS} = -4,5 \text{ V}$$

$$V_{DS} = V_D - V_S = 5,5 \text{ V}$$

b)

$$R_D \parallel R_L \cdot i_d + r_o \cdot i_d - \mu \cdot v_{gs} + R_S \cdot i_d = 0$$

$$v_{gs} = v_g - i_d \cdot R_S$$


$$v_{iz} = -R_D \parallel R_L \cdot i_d$$

$$R_D \parallel R_L \cdot i_d + r_o \cdot i_d - \mu \cdot v_g + \mu \cdot i_d \cdot R_S + R_S \cdot i_d = 0$$

$$i_d = \frac{\mu \cdot v_g}{R_D \parallel R_L + r_o + (\mu + 1) \cdot R_S}$$

$$v_{iz} = \frac{-R_D \parallel R_L \cdot \mu \cdot v_g}{R_D \parallel R_L + r_o + (\mu + 1) \cdot R_S}$$
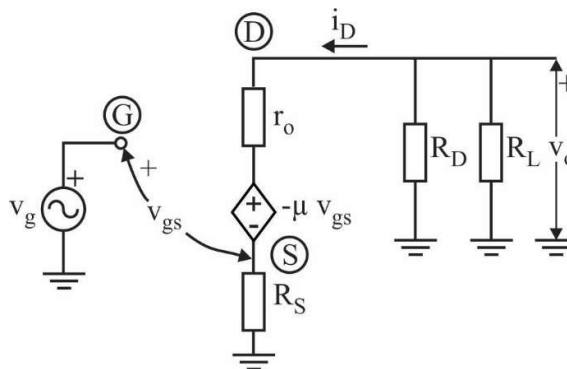
$$A_n = \frac{v_{iz}}{v_g} = -\frac{R_D \parallel R_L \cdot \mu}{R_D \parallel R_L + r_o + (\mu + 1) \cdot R_S} = -1,96$$



c)

$$r_o \cdot i_d - \mu \cdot v_{gs} + R_S \cdot i_d = v_o$$

$$v_{gs} = -i_d \cdot R_S$$

$$i_o = i_d + \frac{v_o}{R_D}$$


$$i_d = \frac{v_o}{r_o + (\mu + 1) \cdot R_S}$$

$$R_{izt} = \frac{v_o}{i_d}$$

$$R_{izt} = r_o + (\mu + 1) \cdot R_S = 75 \text{ k}\Omega$$

$$i_o = \frac{v_o}{R_{izt}} + \frac{v_o}{R_D}$$
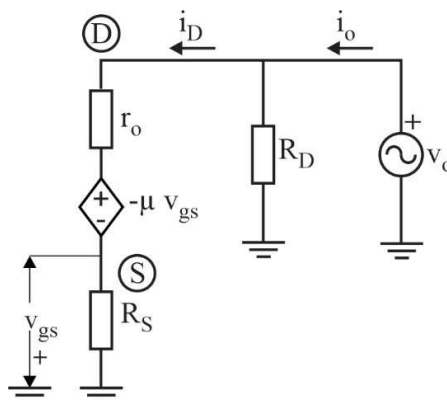
$$R_{iz} = \frac{v_o}{i_o} = \frac{1}{\frac{1}{R_{izt}} + \frac{1}{R_D}} = R_{izt} \parallel R_D = 1,94 \text{ k}\Omega$$




3. Zadatak

Parametri tranzistora u kolu sa slike su: $V_{BE} = -0,6 \text{ V}$; $h_{21E} = \beta = 90$; $h_{22E} = 0 \text{ S}$.

$V_{CC} = 12 \text{ V}$; $V_{EE} = 12 \text{ V}$; $R_E = 10 \text{ k}\Omega$; $R_S = 200 \Omega$; $R_C = 6 \text{ k}\Omega$; $R_L = 12 \text{ k}\Omega$;

$C_{C1} = 1 \mu\text{F}$ $C_{C2} = 0,2 \mu\text{F}$.

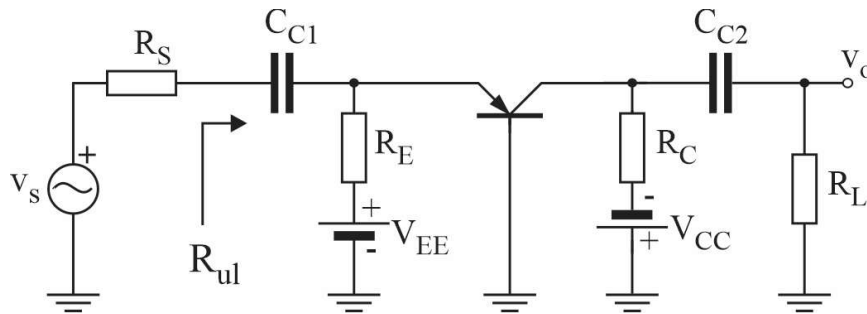- dinamički parametre tranzistora, $h_{11E} = r_\pi$;
- ulaznu otpornost R_{ul} ;
- pojačanje na srednjim frekvencijama (za $C_{C1} \rightarrow \infty$, $C_{C2} \rightarrow \infty$);
- donju graničnu frekvenciju pojačavača;
- skicirati asimptotsku aproksimaciju amplitudske karakteristike ukoliko se usvoji da je $C_{C2} \rightarrow \infty$ (uzima se u obzir samo dominantni pol).



Rešenje:

a)

$$V_E = -V_{BE}$$

$$I_E = \frac{V_{EE} - V_E}{R_E} = \frac{V_{EE} + V_{BE}}{R_E} = 1,14 \text{ mA}$$

$$I_B = \frac{I_E}{\beta + 1} = 12,5 \mu\text{A}$$


$$h_{11E} = \frac{V_T}{I_B} = \frac{26 \text{ mV}}{12,5 \mu\text{A}} = 2,08 \text{ k}\Omega$$

b)

Odredjivanje ulazne otpornosti R_{in}

$$-i_{int} - i_b - h_{21E} \cdot i_b = 0$$

$$i_b = -\frac{v_{in}}{h_{11E}}$$

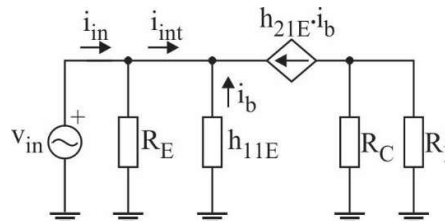


$$R_{int} = \frac{v_{in}}{i_{int}} = \frac{h_{11E}}{1 + h_{21}} = 23 \Omega$$

$$R_{in} = \frac{v_{in}}{i_{in}} = R_E \parallel R_{int} \approx R_{int}$$

$$R_{in} \approx 23 \Omega$$

c)

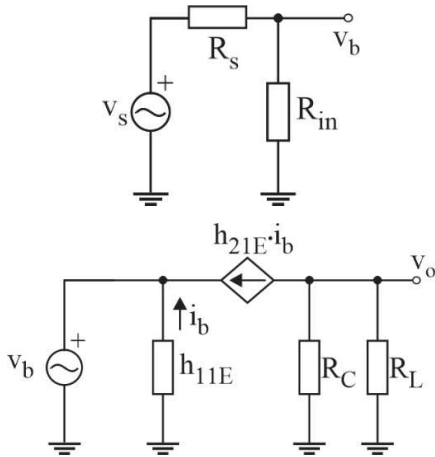pojačanje na srednjim frekvencijama (za $C_{C1} \rightarrow \infty, C_{C2} \rightarrow \infty$)



$$v_b = \frac{R_{in}}{R_{in} + R_s} v_s$$

$$v_o = -h_{21E} R_C \parallel R_L$$


$$i_b = -\frac{v_b}{h_{11E}}$$

$$A_{no} = \frac{v_o}{v_s} = \frac{h_{21E} R_C \parallel R_L}{h_{11E}} \frac{R_{in}}{R_{in} + R_s}$$


$$A_{no} = 18,56$$

d)

Određivanje donje granične frekvencije

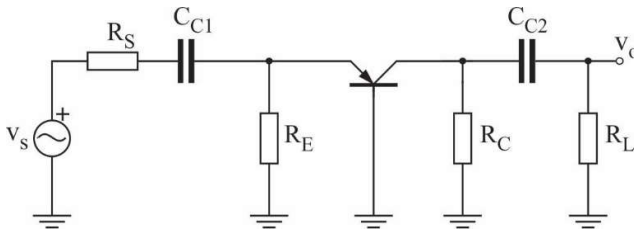


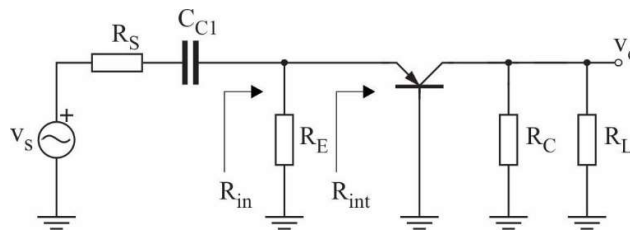- Vremenska konstanta koja odgovara kondenzatoru C_{C1} , τ_1 određuje se iz kola koje je dole prikazano.




$$\tau_1 = C_{C1} \cdot (R_s + R_{in}) = 2,23 \cdot 10^{-4} \text{ s}$$

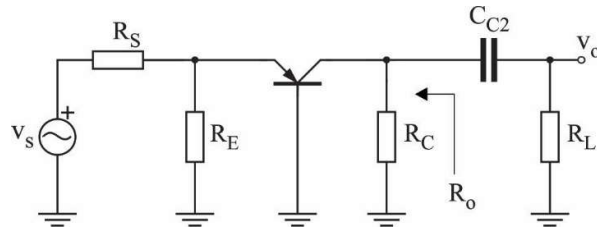- Vremenska konstanta koja odgovara kondenzatoru C_{C2} , τ_2 određuje se iz dole prikazanog kola.



Odredjivanje izlazne otpornosti R_o

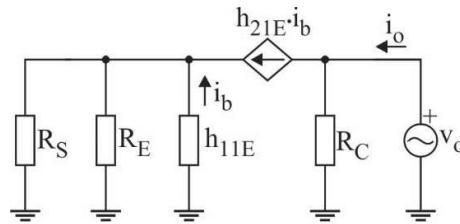

$$R_o = R_C$$

$$\tau_2 = C_{C2} \cdot (R_o + R_L) = 3,6 \cdot 10^{-3} \text{ s}$$

Donja granična frekvencija kola određuje se preko vremenskih konstanti:

$$\omega_d \approx \frac{1}{\tau_1} + \frac{1}{\tau_2} = 4760 \frac{\text{rad}}{\text{s}}$$


$$f_d = \frac{\omega_d}{2\pi} = 758 \text{ Hz}$$

e)

$$A(s) = A_{n0} \frac{s\tau_1}{1 + s\tau_1} = A_o \frac{\frac{s}{\omega_{z1}}}{1 + \frac{s}{\omega_{p1}}}$$

$$\omega_{p2} = \omega_z = 4484 \frac{\text{rad}}{\text{s}}$$

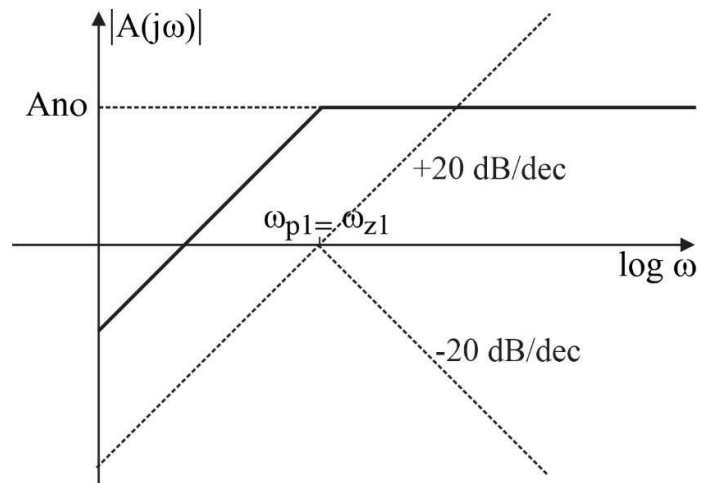
$$A_o = 20 \log_{10} 18,56 = 12 \text{ dB}$$



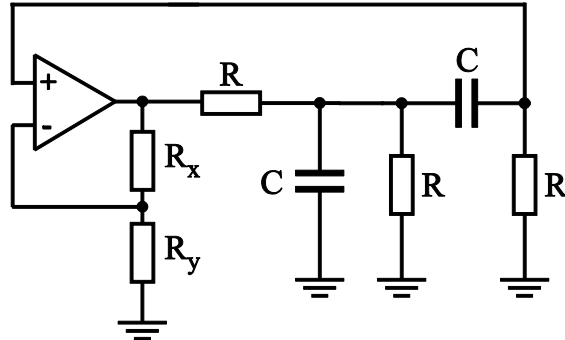
4. Zadatak

Za kolo oscilatora prikazano na slici 4 poznato je $C=10 \text{ nF}$; $R = 1 \text{ k}\Omega$; $R_y = 5 \text{ k}\Omega$. Operacioni pojačavači su idealni. Odrediti:

- Analitički izraz kružnog pojačanja;
- Otpornost R_x tako da nastanu oscilacije;
- Frekvenciju oscilacija kada je ispunjen uslov oscilovanja.



Rešenje:

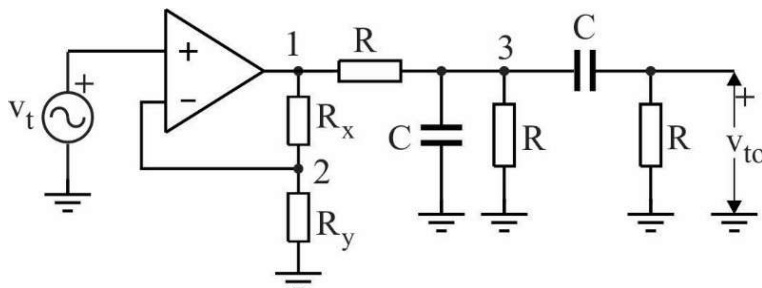

$$\begin{aligned} \frac{V_2}{R_1} + (V_2 - V_1) \frac{1}{R_x} &= 0 \\ \frac{V_3}{R} + V_3 sC + \frac{V_3 - V_1}{R} + (V_3 - V_{to})sC &= 0 \\ \frac{V_{to}}{R} + (V_{to} - V_3)sC &= 0 \\ V_2 &= V_t \end{aligned}$$

$$AB = \frac{V_{to}}{V_t} = \frac{sCR(R_x + R_y)}{2R_y + 4sCRR_y + s^2C^2R^2R_y}$$

Iz uslova $AB = 1 + j0$ dobija se:

$$2R_y + 4j\omega CRR_y - \omega^2 C^2 R^2 R_y = j\omega CR_x R + j\omega CR_y R$$

Realni deo jednačine

$$2R_y - \omega^2 C^2 R^2 R_y = 0$$

$$\omega_o = \frac{\sqrt{2}}{CR} = 141\,000 \frac{\text{rad}}{\text{s}}$$

$$f_o = \frac{\omega_o}{2\pi} = 22,4 \text{ kHz}$$

Imaginarni deo jednačine

$$4j\omega CRR_y - j\omega CR_x R - j\omega CR_y R = 0$$

$$3R_y - R_x = 0$$

$$R_x = 3R_y = 15 \text{ k}\Omega$$